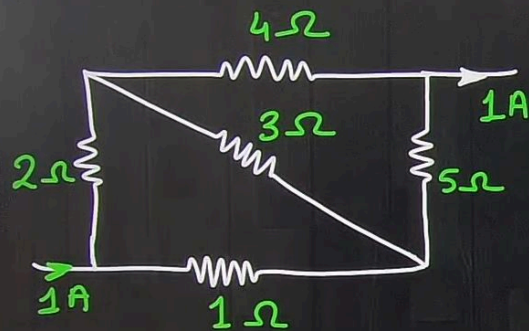


When circuit is
complete, use KVL

When circuit is open,
use KCL



By using Kirchhoff's laws, calculate branch currents in the circuit.





mesh wise.

① Assume direction to apply KVL.

II.

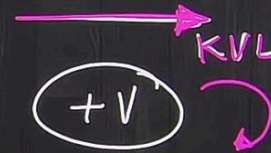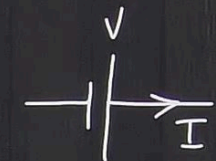

III.

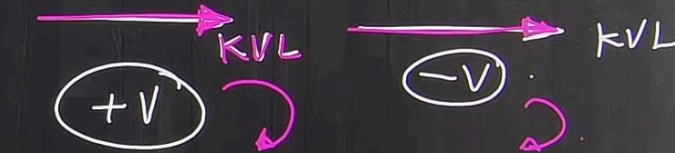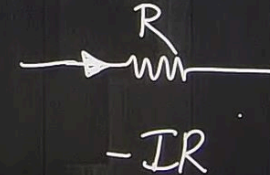

IV.


Assume proper currents.

By using Kirchhoff's laws, calculate branch currents in the circuit.

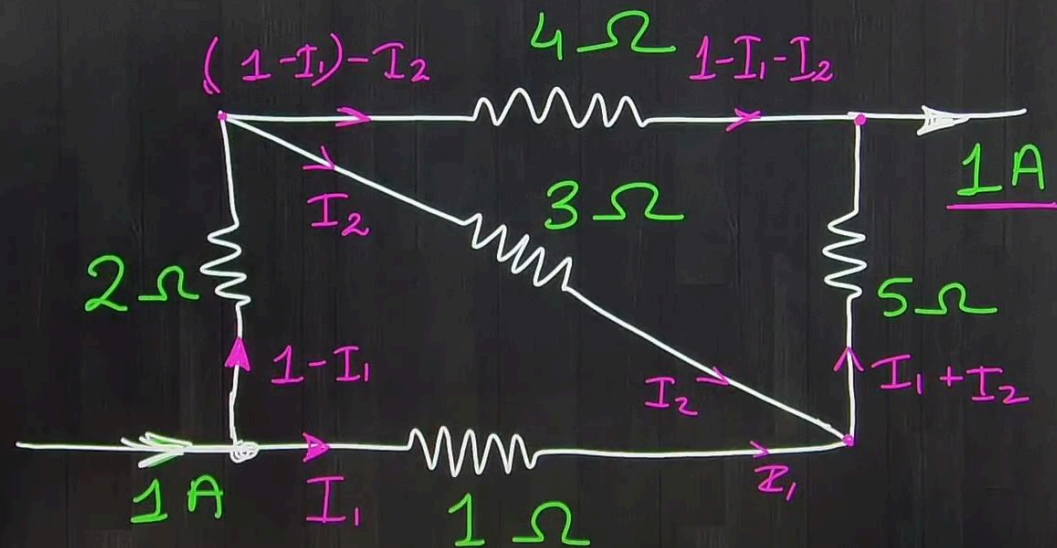08:16


$$(1 - I_1 - I_2) + (I_1 + I_2)$$

$$\textcircled{1} - I_1 - I_2 + I_1 + I_2$$



laws, calculate
circuit.

Apply KVL to ABDA.

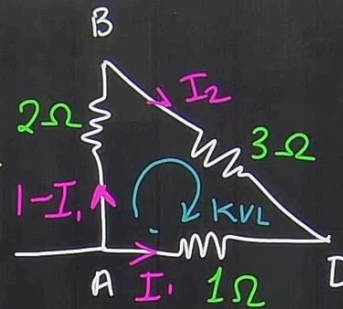



$$-[(1-I_1)2] - I_2 3 - (-I_1 1) = 0$$

$$-2(1-I_1) - 3I_2 + I_1 = 0$$

$$-2 + 2I_1 - 3I_2 + I_1 = 0$$

$$3I_1 - 3I_2 = +2 \quad \text{--- (1)}$$

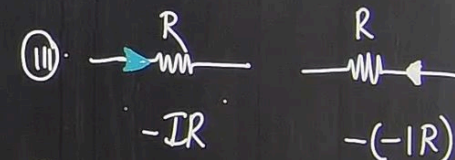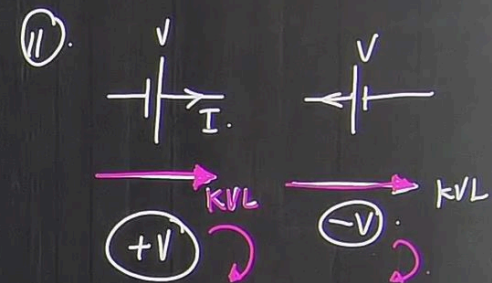mesh wise.
① Assume direction to apply KVL.



④ Assume proper currents.

calculate

Apply KVL to ABDA


$$\begin{aligned}
 & -[(1-I_1)2] - I_2 3 - (-I_1 1) \\
 & -2(1-I_1) - 3I_2 + I_1 = 0 \\
 & -2 + 2I_1 - 3I_2 + I_1 = 0
 \end{aligned}$$

$$3I_1 - 3I_2 = +2 \quad \text{--- (1)}$$

Apply KVL to BCDB




$$\begin{aligned}
 & -(1-I_1-I_2)4 - (-(I_1+I_2)5) - (-I_2 3) = 0 \\
 & -4(1-I_1-I_2) + 5(I_1+I_2) + 3I_2 = 0 \\
 & -4 + 4I_1 + 4I_2 + 5I_1 + 5I_2 + 3I_2 = 0
 \end{aligned}$$
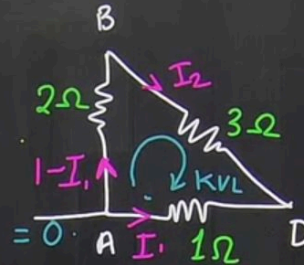
$$9I_1 + 12I_2 = 4 \quad \text{--- (2)}$$




mesh wise. 08:36

① Assume direction to apply KVL.

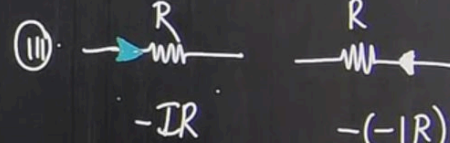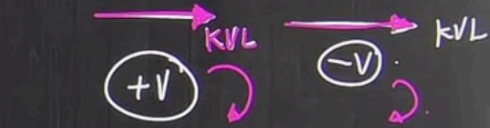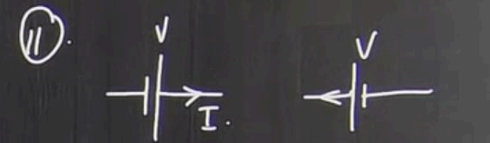

④ Assume proper currents.

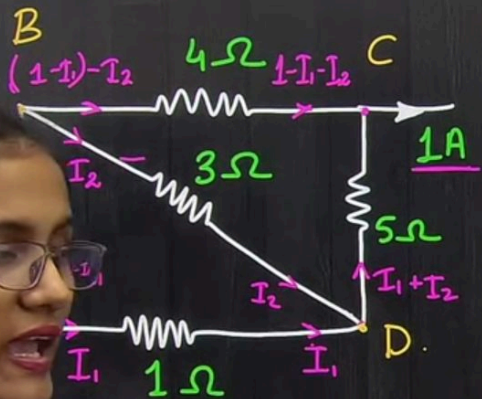By using Kirchhoff's laws, calculate branch currents in the circuit



$$x = I_1 = 0.571$$

$$y = I_2 = -0.095$$

Apply KVL to ABDA

$$-[(1-I_1)2] - I_2 3 - (-I_1 1)$$

$$-2(1-I_1) - 3I_2 + I_1 = 0$$

$$-2 + 2I_1 - 3I_2 + I_1 = 0$$

$$3I_1 - 3I_2 = +2 \quad \text{--- (1)}$$



Apply KVL to BCDB

$$-(1-I_1-I_2)4 - (-(I_1+I_2)5) - (-I_2 3) = 0$$

$$-4(1-I_1-I_2) + 5(I_1+I_2) + 3I_2 = 0$$

$$-4 + 4I_1 + 4I_2 + 5I_1 + 5I_2 + 3I_2 = 0$$
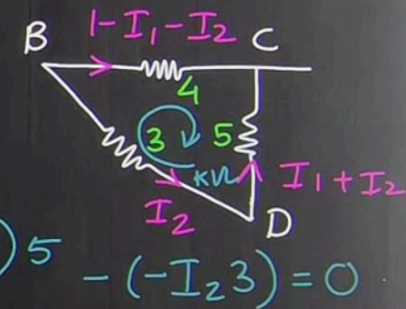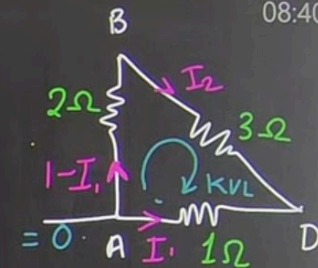
$$9I_1 + 12I_2 = 4 \quad \text{--- (2)}$$



Apply KVL to ABDA

$$-[(1-I_1)2] - I_2 3 - (-I_1 1)$$

$$-2(1-I_1) - 3I_2 + I_1 = 0$$

$$-2 + 2I_1 - 3I_2 + I_1 = 0$$

$$3I_1 - 3I_2 = +2 \quad \text{--- (1)}$$



Apply KVL to BCDB

$$-(1-I_1-I_2)4 - (-(I_1+I_2)5) - (-I_2 3) = 0$$

$$-4(1-I_1-I_2) + 5(I_1+I_2) + 3I_2 = 0$$

$$-4 + 4I_1 + 4I_2 + 5I_1 + 5I_2 + 3I_2 = 0$$
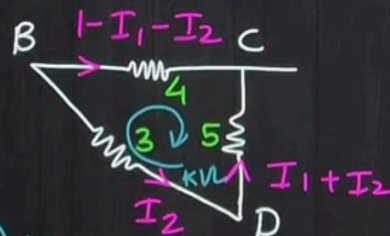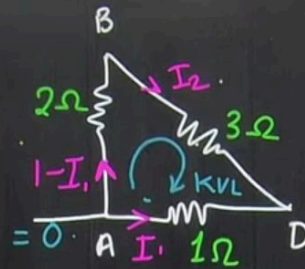
$$9I_1 + 12I_2 = 4 \quad \text{--- (2)}$$



$$\begin{aligned} \text{branch AB} &= 1 - I_1 \\ &= 1 - 0.571 \\ &= \underline{\hspace{2cm}} \end{aligned}$$

$$\begin{aligned} BD &= I_2 \\ &= \underline{\hspace{2cm}} \end{aligned}$$

$$\begin{aligned} AD &= I_1 \\ &= \underline{\hspace{2cm}} \end{aligned}$$

① A

②

③

④

to ABDA

$$-I_2 \cdot 3 - (-I_1 \cdot 1)$$

$$-3I_2 + I_1 = 0$$

$$3I_2 + I_1 = 0$$

$$-3I_2 = +2 \quad \text{--- (1)}$$


KVL to BCDB

$$-I_2 \cdot 4 - (-(I_1 + I_2) \cdot 5) - (-I_2 \cdot 3) = 0$$

$$-I_2 + 5(I_1 + I_2) + 3I_2 = 0$$

$$+4I_2 + 5I_1 + 5I_2 + 3I_2 = 0$$

$$1 + 12I_2 = 4 \quad \text{--- (2)}$$

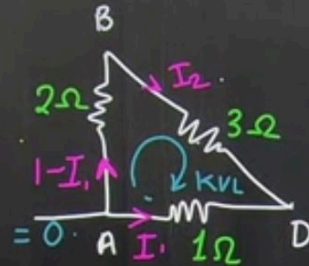

$$\begin{aligned} \text{branch AB} &= 1 - I_1 \\ &= 1 - 0.571 \\ &= \underline{0.429 \text{ A}} \end{aligned}$$

$$\begin{aligned} BD &= I_2 \\ &= \underline{-0.0952} \end{aligned}$$



$$\begin{aligned} AD &= I_1 \\ &= \underline{0.571} \end{aligned}$$

$$\begin{aligned} BC &= 1 - I_1 - I_2 \\ &= \underline{1 - 0.571 - (-0.0952)} \end{aligned}$$

$$\begin{aligned} CD &= I_1 + I_2 \\ &= \underline{0.571 + (-0.0952)} \\ &= \underline{0.5242} \end{aligned}$$


08:45

① Assumption

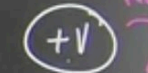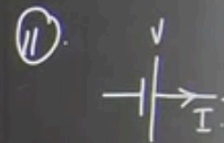

④ Assume p

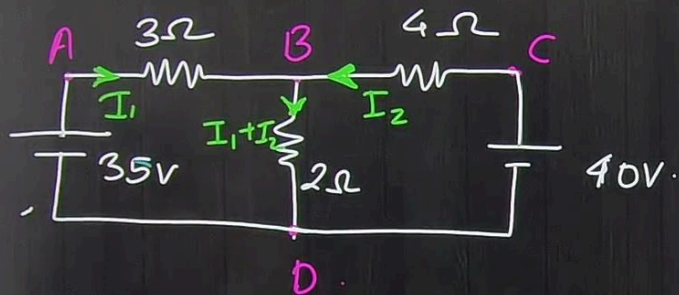By using kirchhoff's law
calculate current in branch.



Current in 2Ω
 $= -I_1 + I_2$
 $= 5 + 5 = 10A //$

$$\begin{cases} I_1 = 5A \\ I_2 = 5A \end{cases}$$

Apply KVL to mesh ABDA

$$\begin{aligned} +35 - 3I_1 - 2(I_1 + I_2) &= 0 \\ -3I_1 - 2I_1 - 2I_2 &= -35 \\ -5I_1 - 2I_2 &= -35 \quad \text{--- (1)} \end{aligned}$$


Apply KVL to mesh BCDB:

$$\begin{aligned} 4I_2 - 40 + 2(I_1 + I_2) &= 0 \\ 4I_2 - 40 + 2I_1 + 2I_2 &= 0 \\ 2I_1 + 6I_2 &= 40 \quad \text{--- (2)} \end{aligned}$$


09:04

Determine the current through
 20Ω resistor in the circuit shown.

09:27

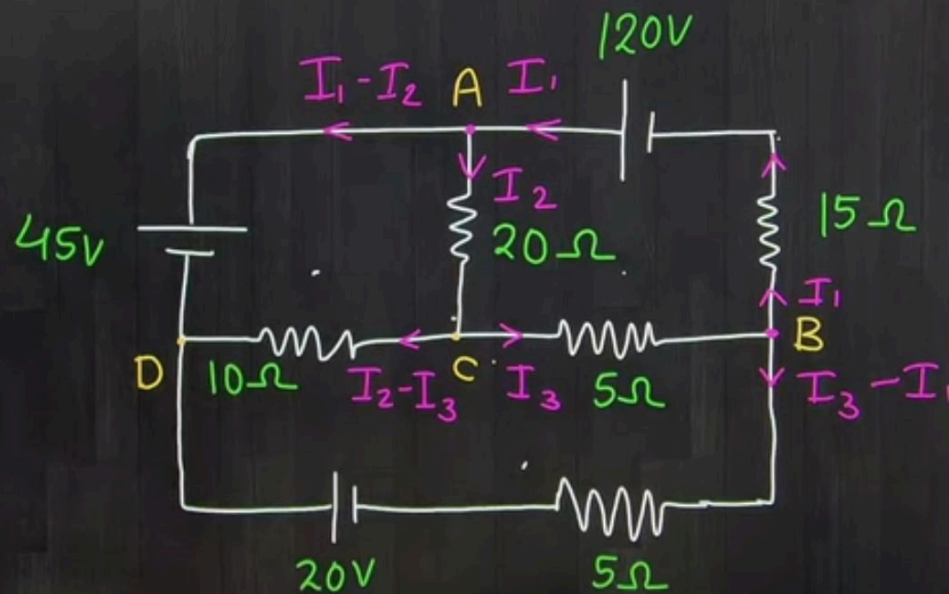

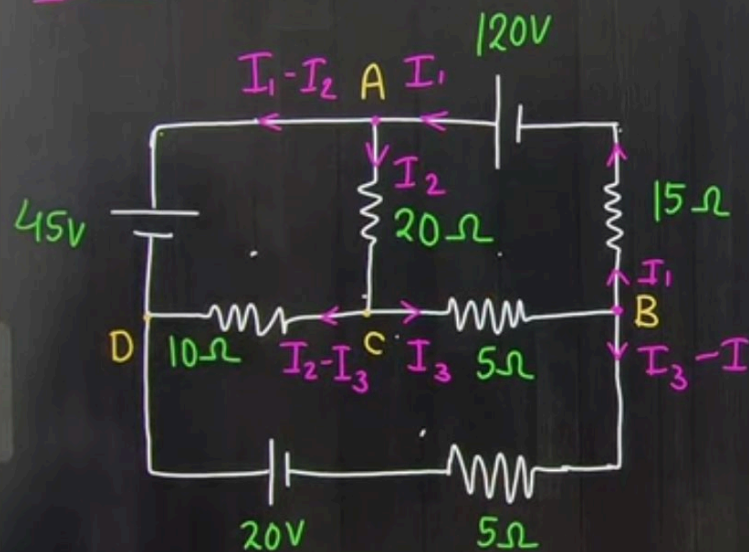Determine the current through
20 Ω resistor in the circuit shown.



Apply KVL to ACDA.

$$-20I_2 - 10(I_2 - I_3) + 45 = 0$$



$$-20I_2 - 10I_2 + 10I_3 = -45$$


$$-30I_2 + 10I_3 = -45 \quad \text{--- (1)}$$

Apply KVL to ABCA

$$-120 + 15I_1 + 5I_3 + 20I_2 = 0$$
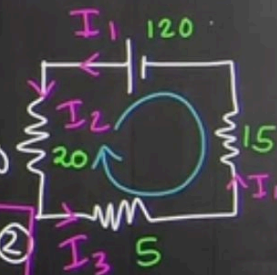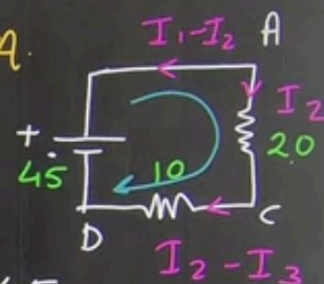
$$15I_1 + 20I_2 + 5I_3 = 120 \quad \text{--- (2)}$$



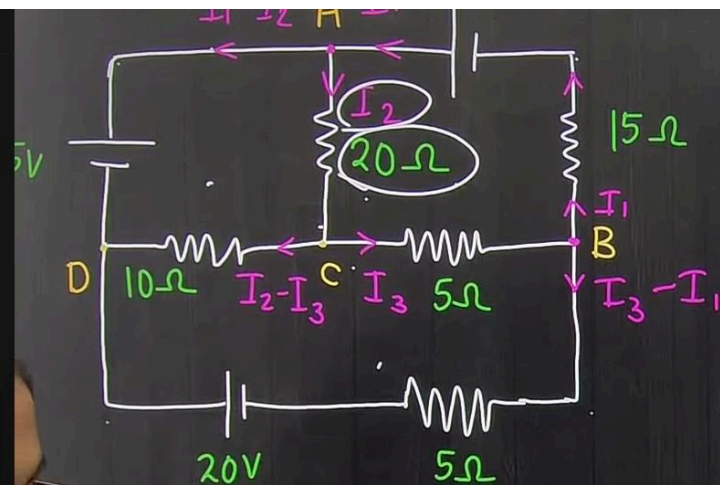

$$\begin{aligned} x = I_1 &= 3.540 \text{ A} \\ y = I_2 &= 2.554 \text{ A} \\ z = I_3 &= 3.162 \text{ A} \end{aligned}$$

Current in $20\Omega = I_2$
 $= 2.554 \text{ A}$

$$-20I_2 - 10I_2 + 10I_3 = -45$$

$$0I_1 - 30I_2 + 10I_3 = -45 \quad \text{--- (1)}$$

Apply KVL to ABCA

$$-120 + 15I_1 + 5I_3 + 20I_2 = 0$$

$$15I_1 + 20I_2 + 5I_3 = 120 \quad \text{--- (2)}$$

Apply KVL to BDCB

$$10(I_2 - I_3) - 5I_3 - 5(I_3 - I_1) + 20 = 0$$

$$10I_2 - 10I_3 - 5I_3 - 5I_3 + 5I_1 = -20$$

$$5I_1 + 10I_2 - 20I_3 = -20$$

