

# Measurement of power in 3 phase circuit/system:


\* Two wattmeter method

$$(1) \tan \phi = \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2}$$

$$(2) \cos \phi = \frac{1 + \gamma}{2\sqrt{1 - \gamma + \gamma^2}} \quad (\text{Power factor})$$

# Measurement of power in 3 phase circuit/system:


\* Two wattmeter method

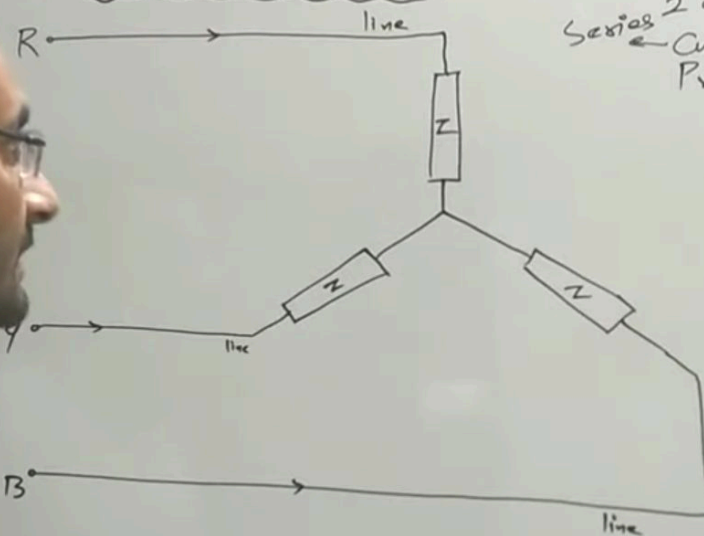

Power  
2 coils  
Series ← Current coil -  $I$   
Pres/Voltage coil -  $V$  }  $P = VI \cos \phi$

# # Measurement of power in 3 phase circuit/system:


## \* Two wattmeter method

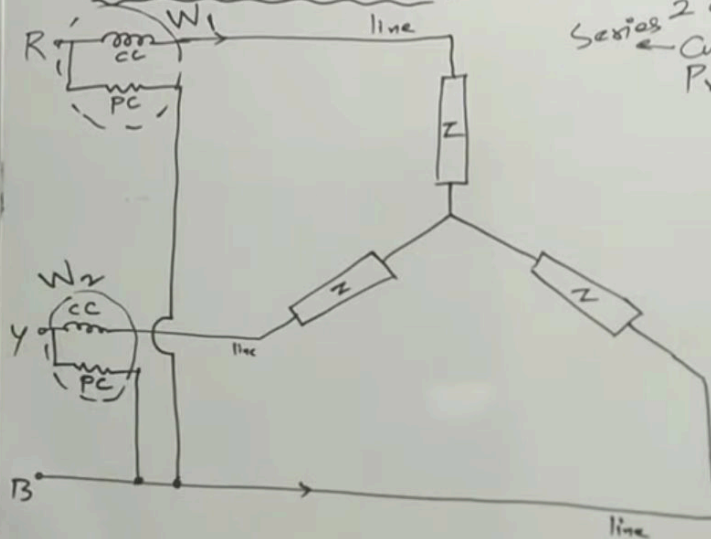

Power  
2 coils  
Series ← Current coil - I  
Parallel ← Pres/Voltage coil - V  
$$P = VI \cos \phi$$


# # Measurement of power in 3 phase circuit/system:

## \* Two wattmeter method

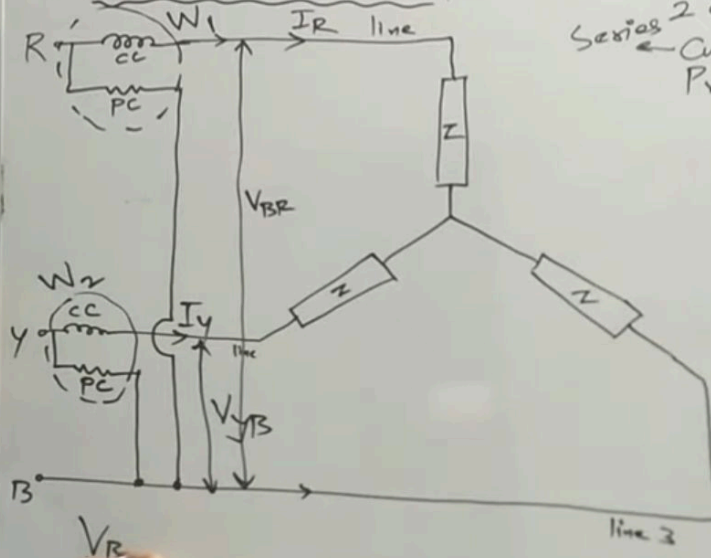

Power 2 coils  
Series ← Current coil -  $I$   
Parallel ← Pres/Voltage coil -  $V$   
}  $P = VI \cos \phi$   
(Parallel)
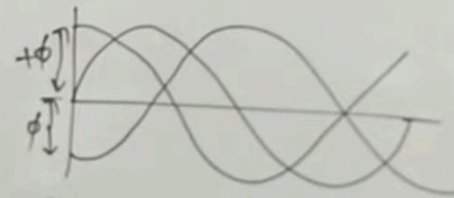
$$W_1 = V_{BR} I_R \cos(30^\circ - \phi) \quad \text{--- (1)}$$




$$W_2 = V_{YB} \cdot I_Y \cos(30^\circ + \phi) \quad \text{--- (2)}$$

$V_R$

# # Measurement of power in 3 phase circuit/system:

## \* Two wattmeter method

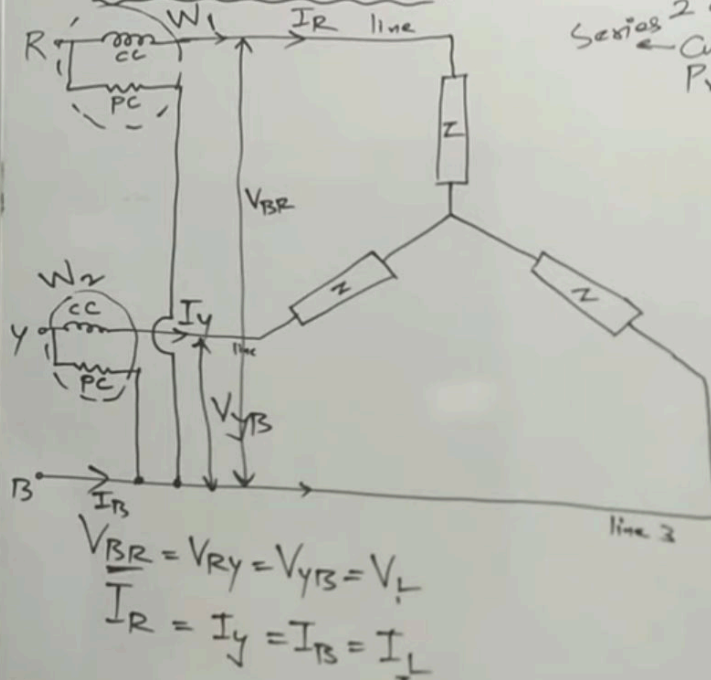


Power 2 coils  
 Series ← Current coil -  $I$   
 Parallel ← Pres/Voltage coil -  $V$   
 $P = VI \cos \phi$

$$W_1 = V_L I_L \cos(30 - \phi)$$

$$W_2 = V_L I_L \cos(30 + \phi)$$
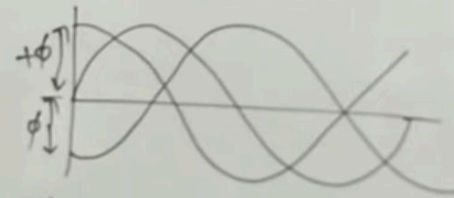
$$W_1 = V_{BR} I_R \cos(30 - \phi) \quad \text{--- (1)}$$



$$W_2 = V_{YB} \cdot I_Y \cos(30 + \phi) \quad \text{--- (2)}$$



# Measurement of power in 3 phase circuit/system:

$$W_1 + W_2 = V_L I_L \cos(30^\circ - \phi) + V_L I_L \cos(30^\circ + \phi)$$

$$= V_L I_L [\cos(30^\circ - \phi) + \cos(30^\circ + \phi)]$$

$$= V_L I_L (\cos 30^\circ \cos \phi + \sin 30^\circ \sin \phi + \cos 30^\circ \cos \phi - \sin 30^\circ \sin \phi)$$

$$= V_L I_L (2 \cos 30^\circ \cos \phi)$$

$$= V_L I_L (2 \times \frac{\sqrt{3}}{2} \cos \phi)$$

$$\underline{W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi} \quad \text{--- (1)}$$

$$W_1 - W_2 = V_L I_L \cos(30^\circ - \phi) - V_L I_L \cos(30^\circ + \phi)$$

$$= V_L I_L [\cos(30^\circ - \phi) - \cos(30^\circ + \phi)]$$

$$= V_L I_L [\cos 30^\circ \cos \phi + \sin 30^\circ \sin \phi - (\cos 30^\circ \cos \phi - \sin 30^\circ \sin \phi)]$$

$$= V_L I_L [\cos 30^\circ \cos \phi + \sin 30^\circ \sin \phi - \cos 30^\circ \cos \phi + \sin 30^\circ \sin \phi]$$

$$= V_L I_L [2 \sin 30^\circ \sin \phi]$$

$$= V_L I_L [2 \times \frac{1}{2} \sin \phi]$$

$$\underline{W_1 - W_2 = V_L I_L \sin \phi} \quad \text{--- (2)}$$

$$W_1 = V_L I_L \cos(30^\circ - \phi)$$

$$W_2 = V_L I_L \cos(30^\circ + \phi)$$

# Measurement of power in 3 phase circuit/system:

$$W_1 + W_2 = V_L I_L \cos(30^\circ - \phi) + V_L I_L \cos(30^\circ + \phi)$$

$$= V_L I_L [\cos(30^\circ - \phi) + \cos(30^\circ + \phi)]$$

$$= V_L I_L (\cos 30^\circ \cos \phi + \sin 30^\circ \sin \phi + \cos 30^\circ \cos \phi - \sin 30^\circ \sin \phi)$$

$$= V_L I_L (2 \cos 30^\circ \cos \phi)$$

$$= V_L I_L (2 \times \frac{\sqrt{3}}{2} \cos \phi)$$

$$\underline{W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi} \quad \text{--- (1)}$$

$$W_1 = V_L I_L \cos(30^\circ - \phi)$$

$$W_2 = V_L I_L \cos(30^\circ + \phi)$$

$$\text{(2) } \frac{W_1 - W_2}{W_1 + W_2} = \frac{V_L I_L \sin \phi}{\sqrt{3} V_L I_L \cos \phi}$$

$$\frac{W_1 - W_2}{W_1 + W_2} = \frac{\tan \phi}{\sqrt{3}}$$

$$\boxed{\tan \phi = \frac{\sqrt{3} (W_1 - W_2)}{W_1 + W_2}}$$

$$W_1 - W_2 = V_L I_L \cos(30^\circ - \phi) - V_L I_L \cos(30^\circ + \phi)$$

$$= V_L I_L [\cos(30^\circ - \phi) - \cos(30^\circ + \phi)]$$

$$= V_L I_L [\cos 30^\circ \cos \phi + \sin 30^\circ \sin \phi - (\cos 30^\circ \cos \phi - \sin 30^\circ \sin \phi)]$$

$$= V_L I_L [\cos 30^\circ \cos \phi + \sin 30^\circ \sin \phi - \cos 30^\circ \cos \phi + \sin 30^\circ \sin \phi]$$

$$= V_L I_L [2 \sin 30^\circ \sin \phi]$$

$$= V_L I_L [2 \times \frac{1}{2} \sin \phi]$$

$$\underline{W_1 - W_2 = V_L I_L \sin \phi} \quad \text{--- (2)}$$

# Measurement of power in 3 phase circuit/system:

$$\begin{aligned} \cos \phi &= \frac{1}{\sec \phi} \\ \frac{W_2}{W_1} &= x \\ \text{ratio of wattmeter reading} &= \frac{1}{\sqrt{\sec^2 \phi}} \\ &= \frac{1}{\sqrt{1 + \tan^2 \phi}} \\ &= \frac{1}{\sqrt{1 + 3 \left( \frac{W_1 - W_2}{W_1 + W_2} \right)^2}} \\ &= \frac{1}{\sqrt{1 + 3x \frac{W_1 \left( 1 - \frac{W_2}{W_1} \right)^2}{W_1 \left( 1 + \frac{W_2}{W_1} \right)^2}}} \\ &= \frac{1}{\sqrt{1 + 3 \left( \frac{1 - \frac{W_2}{W_1}}{1 + \frac{W_2}{W_1}} \right)^2}} \\ &= \frac{1}{\sqrt{1 + 3 \left( \frac{1 - x}{1 + x} \right)^2}} \end{aligned}$$

$$\begin{aligned} \cos \phi &= \frac{1}{\sqrt{\frac{1(1+x)^2 + 3(1-x)^2}{(1+x)^2}}} \quad \left[ \tan \phi = \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} \right] \\ \cos \phi &= \frac{\sqrt{(1+x)^2}}{\sqrt{(1+x)^2 + 3(1-x)^2}} \\ \cos \phi &= \frac{(1+x)}{\sqrt{1 + 2x + x^2 + 3(1 - 2x + x^2)}} \\ \cos \phi &= \frac{(1+x)}{\sqrt{1 + 2x + x^2 + 3 - 6x + 3x^2}} \\ \cos \phi &= \frac{(1+x)}{\sqrt{4 - 4x + 4x^2}} \\ \cos \phi &= \frac{1+x}{2\sqrt{1-x+x^2}} \\ \text{Power factor} & \end{aligned}$$



Q) Two wattmeters are connected to measure 3 phase power for the Star connected loads  $10.37 \text{ W}$  &  $5.185 \text{ W}$ . The line current is  $10 \text{ A}$ . Calculate (i) Line and phase voltages, (ii) Impedance & Resistance.

$$\tan \phi = \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$I_L = I_{ph} = 10 \text{ A}$$

$$V_L = \sqrt{3} V_{ph}$$

$$W_1 = 10.37 \text{ W}$$

$$W_2 = 5.185 \text{ W}$$

$$\left. \begin{array}{l} V_L \\ V_{ph} \\ Z \\ R \end{array} \right\}$$

$$\cos \phi = \frac{R}{Z}$$

Q) Two wattmeters are connected to measure 3 phase power for the Star connected loads 10.37 W & 5.185 W. The line current is 10 A. Calculate (i) Line and phase voltages, (ii) Impedance & Resistance.

Sol<sup>n</sup>  

$$\Rightarrow \tan \phi = \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} = \frac{\sqrt{3}(10.37 - 5.185)}{(10.37 + 5.185)}$$

$$\tan \phi = 0.57735$$

$$\phi = \tan^{-1}(0.57735)$$

$$\phi = 30$$

Power factor  $\cos \phi \rightarrow \cos(30)$   
 $\cos \phi = 0.8660$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$15.555 = \sqrt{3} \times V_L \times 10 \times 0.8660$$

$$V_L = \frac{15.555}{\sqrt{3} \times 10 \times 0.8660}$$

$$V_L = 1.03 \text{ Volt} \quad \underline{\text{Ans}}$$

$$V_L = \sqrt{3} V_{ph}$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{1.03}{\sqrt{3}}$$

$$V_{ph} = 0.59 \text{ Volts} \quad \underline{\text{Ans}}$$

$$\tan \phi = \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2}$$

$$P = W_1 + W_2 \quad P = \sqrt{3} V_L I_L \cos \phi$$

$$= 10.37 + 5.185 \quad I_L = I_{ph} = 10 \text{ A}$$

$$P = 15.555 \text{ W}$$

$$V_{ph} = I_{ph} Z$$

$$Z = \frac{V_{ph}}{I_{ph}}$$

$$= \frac{0.59}{10}$$

$$Z = 0.059 \Omega$$

$$\cos \phi = \frac{R}{Z}$$

$$R = \cos \phi Z$$


$$= 0.8660 \times 0.059$$

$$R = 0.051 \Omega \quad \underline{\text{Ans}}$$

$$V_L = \sqrt{3} V_{ph}$$

$$W_1 = 10.37 \text{ W}$$

$$W_2 = 5.185 \text{ W}$$

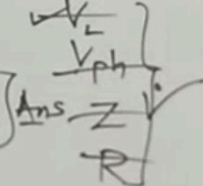

$$\cos \phi = \frac{R}{Z}$$