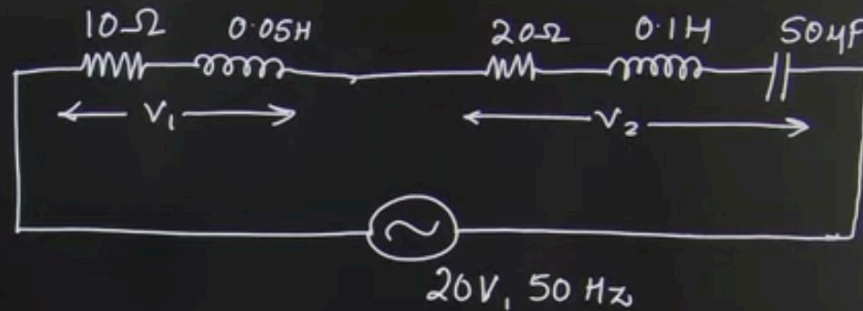


For a circuit shown in figure

i) find current

ii) Voltage drop  $V_1$

iii) Voltage drop  $V_2$




For a circuit shown in figure

i) find current

ii) Voltage drop  $V_1$

iii) Voltage drop  $V_2$

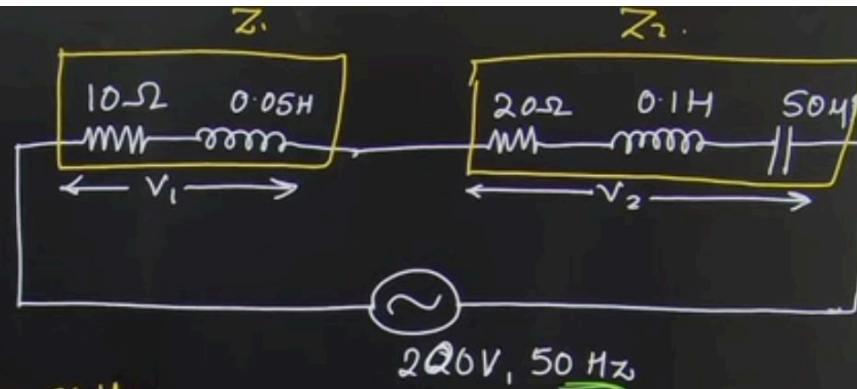

Given data.  $V = (200, \angle 0^\circ)$   $f = 50\text{ Hz}$

$$R_1 = 10\Omega \quad R_2 = 20\Omega$$

$$R = R_1 + R_2 = 10 + 20 = 30\Omega$$

$$L_1 = 0.05H \quad L_2 = 0.1H$$

$$X_{L1} = \omega L_1$$

$$= 2\pi f \cdot L_1$$

$$= 2 \times \pi \times 50 \times 0.05$$

$$X_{L1} = 15.71\Omega$$

$$X_{L2} = 2\pi f L_2$$

$$= 2 \times \pi \times 50 \times 0.1$$

$$X_{L2} = 31.42\Omega$$

$$C = 50\mu F$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$= \frac{1}{2 \times \pi \times 50 \times 50 \times 10^{-6}}$$


$$X_C = 63.66\Omega$$

For a circuit shown in figure

i) find current =  $\frac{\text{Total } V}{\text{Total } Z}$

ii) Voltage drop  $V_1$

iii) Voltage drop  $V_2$

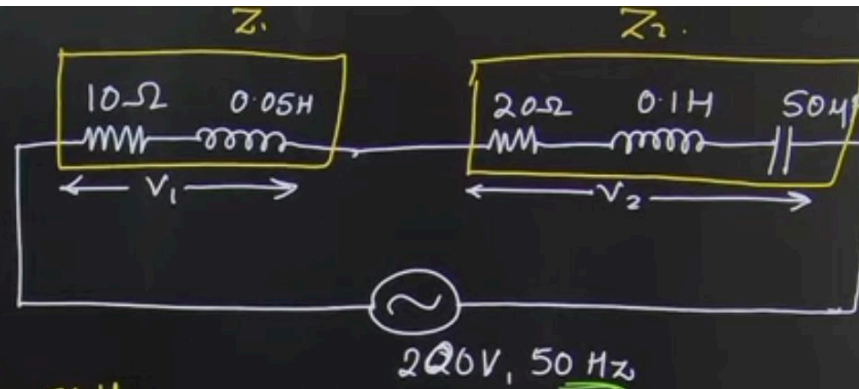

Given data.  $V = 220V$ ,  $f = 50 \text{ Hz}$

$R_1 = 10 \Omega$ ,  $R_2 = 20 \Omega$

$R = 10 + 20 = 30 \Omega$

$L_1 = 0.05 \text{ H}$   
 $X_L$

$X_L = 2\pi f L_1$   
 $= 2\pi \times 50 \times 0.05$   
 $= 15.71 \Omega$

$C = 50 \mu\text{F}$

$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$

$= \frac{1}{2\pi \times 50 \times 50 \times 10^{-6}}$

$X_C = 63.66 \Omega$

$X_L = X_{L1} + X_{L2}$   
 $= 15.71 + 31.42$   
 $= 47.13$

$X_C = 63.66 \Omega$

$X_C > X_L$

This is capacitive.

Given data.  $V = (200, \angle 0^\circ)$   $f = 50 \text{ Hz}$

$$R_1 = 10 \Omega \quad R_2 = 20 \Omega$$

$$R = R_1 + R_2 = 10 + 20 = 30 \Omega$$

$$L_1 = 0.05 \text{ H} \quad L_2 = 0.1 \text{ H}$$

$$X_{L1} = \omega L_1$$

$$= 2\pi f \cdot L_1$$

$$= 2 \times \pi \times 50 \times 0.05$$

$$X_{L1} = 15.71 \Omega$$

$$X_{L2} = 2\pi f L_2$$

$$= 2 \times \pi \times 50 \times 0.1$$

$$X_{L2} = 31.42 \Omega$$

$$C = 50 \mu\text{F}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$= \frac{1}{2 \times \pi \times 50 \times 50 \times 10^{-6}}$$

$$X_C = 63.66 \Omega$$

$$X_L = X_{L1} + X_{L2}$$

$$= 15.71 + 31.42$$

$$= 47.13$$

$$X_C = 63.66 \Omega$$

$$X_C > X_L$$

This is capacitive.

$$Z = (R - j(X_C - X_L))$$

$$\bar{Z} = (30 - j16.53) \Omega$$

$$\bar{Z} = (34.25, \angle -28.85^\circ) \Omega$$

$$I = \frac{\bar{V}}{\bar{Z}} = \frac{(200, \angle 0^\circ)}{(34.25, \angle -28.85^\circ)}$$

$$= \left( \frac{200}{34.25} \angle [0 - (-28.85)] \right)$$

$$= (5.84 \angle 28.85^\circ)$$



② Voltage drop  $V_1$

③ Voltage drop  $V_2$

Given data.  $V = (200, \angle 0) \text{ f} = 50 \text{ Hz}$

$$R_1 = 10 \Omega \quad R_2 = 20 \Omega$$

$$R = R_1 + R_2 = 10 + 20 = 30 \Omega$$

200V, 50 Hz

$$L_1 = 0.05 \text{ H} \quad L_2 = 0.1 \text{ H}$$

$$X_{L1} = \omega L_1$$

$$= 2\pi f L_1$$

$$= 2\pi \times 50 \times 0.05$$

$$X_{L1} = 15.71 \Omega$$

$$X_{L2} = 2\pi f L_2$$

$$= 2\pi \times 50 \times 0.1$$

$$X_{L2} = 31.42 \Omega$$

$$X_L = X_{L1} + X_{L2}$$

$$= 15.71 + 31.42$$

$$X_L = 47.13 \Omega$$

$$X_C = \frac{1}{\omega C}$$

$$= \frac{1}{2\pi f C}$$

$$= \frac{1}{2\pi \times 50 \times 50 \times 10^{-6}}$$

$$X_C = 63.66 \Omega$$

$$X_C > X_L$$

$$\text{This is capacitive.}$$

$$Z = (R - j(X_C - X_L))$$

$$\bar{Z} = (30 - j16.53) \Omega$$

$$\bar{Z} = (34.25, \angle -28.85) \Omega$$

$$I = \frac{\bar{V}}{\bar{Z}} = \frac{(200, \angle 0)}{(34.25, \angle -28.85)}$$

$$= \frac{200}{34.25} \angle (0 - (-28.85))$$

$$I = (5.84 \angle 28.85)$$

$$\textcircled{ii} V_1 = I Z_1$$

$$= (5.84 \angle 28.85)(18.62, \angle 57.52)$$

$$= (5.84 \times 18.62, \angle 28.85 + 57.52)$$

$$V_1 = (108.74, \angle 86.37)$$

$$Z_1 = R_1 + jX_{L1}$$

$$\bar{Z} = 10 + j15.71$$

$$\bar{Z} = (18.62, \angle 57.52)$$

$$(11) V_1 = I Z_1$$

$$= (5.84 \angle 28.85)(18.62, 257.52)$$

$$= (5.84 \times 18.62, \angle 28.85 + 57.52)$$

$$V_1 = (108.74, \angle 86.37) \text{ V}$$

$$V_2 = I Z_2$$

$$= (5.84 \angle 28.85)(37.94, \angle -58.19)$$

$$= (5.84 \times 37.94 \angle 28.85 - 58.19)$$

$$V_2 = (221.57, \angle -29.34) \text{ V}$$

$$Z_1 = (R_1 + j(X_L - X_C))$$

$$\bar{Z}_1 = (30 - j16.53) \Omega$$

$$\bar{Z}_1 = (34.25, \angle -28.85) \Omega$$

$$X_L = 63.66 \Omega$$

$$I = \frac{V}{Z} = \frac{(200, \angle 0)}{(34.25, \angle -28.85)}$$

$$= \frac{200}{34.25} \angle (0 - (-28.85))$$

$$I = (5.84 \angle 28.85)$$

$$Z_1 = R_1 + jX_L$$

$$\bar{Z}_1 = 10 + j15.71$$

$$\bar{Z}_1 = (18.62, \angle 57.52)$$

$$\bar{Z}_2 = R_2 - j(X_C - X_L)$$

$$\bar{Z}_2 = 20 - j(63.66 - 31.42)$$

$$= 20 - j(32.24)$$


$$\bar{Z}_2 = (37.94, \angle -58.19)$$

$$I = (5.84 \angle 28.85)$$

An R-L-C series circuit has a current that lags behind the applied voltage by  $45^\circ$ .

The voltage across inductance has a maximum value equal to twice the maximum voltage across the capacitor.

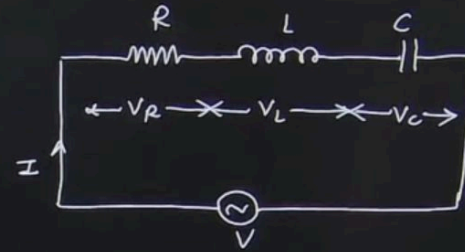
Voltage across the inductance is  $300\sin(1000t)$  and  $R=20\Omega$ . Find values of Inductance and capacitance.



An R-L-C series circuit has a current that lags behind the applied voltage by  $45^\circ$ .

The voltage across inductance has a maximum value equal to twice the maximum voltage across the capacitor.

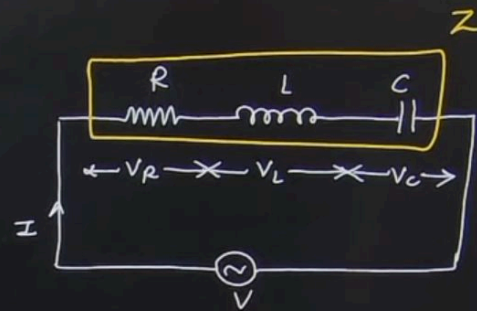Voltage across the inductance is  $300\sin(1000t)$  and  $R = 20\Omega$ . Find values of Inductance and capacitance.



$$\text{power factor} = \cos \phi = \frac{R}{Z}$$

$$\cos 45 = \frac{20}{Z}$$

$$Z = 28.28\Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{20^2 + (2X_C - X_C)^2}$$

$$28.28 = \sqrt{400 + X_C^2}$$

$$X_C = 19.99\Omega$$

$$\boxed{X_C = 20\Omega}$$

Given. Inductive circuit.

$$V_L = 2V_C$$

$$\sqrt{2}V_L = 2 \cdot \sqrt{2}V_C$$

$$V_L = 2 \cdot V_C$$

$$1X_L = 2 \cdot 1X_C$$

$$\boxed{X_L = 2 \cdot X_C}$$

$$\phi = 45^\circ$$

$$V_L = 300\sin(1000t)$$

$$R = 20\Omega$$

$$\omega = 1000$$



maximum voltage across the capacitor.

Voltage across the inductance is  $300\sin(1000t)$   
and  $R = 20\Omega$ . Find values of Inductance and capacitance.

Given. Inductive circuit.

$$V_L = 2V_C$$

$$\sqrt{2}V_L = 2 \cdot \sqrt{2}V_C$$

$$V_L = 2 \cdot V_C$$

$$IX_L = 2 \cdot IX_C$$

$$X_L = 2 \cdot 20$$

$$X_L = 40\Omega$$

$$X_L = 2X_C$$

$$\phi = 45^\circ$$


$$V_L = 300\sin(1000t)$$

$$R = 20\Omega$$

$$\omega = 1000$$

$$X_C = 20\Omega$$

$$Z = 28.28$$

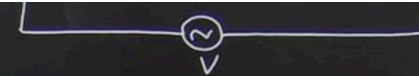

$$\text{power factor} = \cos \phi = \frac{R}{Z}$$

$$\cos 45 = \frac{20}{Z}$$

$$Z = 28.28\Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{20^2 + (2X_C - X_C)^2}$$

$$28.28 = \sqrt{400 + X_C^2}$$

$$X_C = 19.99$$

$$X_C = 20\Omega$$

551-168

$$V_L = 2V_C$$

$$\sqrt{2}V_L = 2 \cdot \sqrt{2}V_C$$

$$V_L = 2 \cdot V_C$$

$$IX_L = 2 \cdot IX_C$$

$$X_L = 2 \cdot 20$$

$$X_L = 40 \Omega$$

$$X_L = 2X_C$$

$$V_L = 300 \sin(1000t)$$

$$R = 20 \Omega$$

$$\omega = 1000$$

$$X_L = 20 \Omega$$

$$\phi = 45^\circ$$

$$Z = 28.28 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{20^2 + (2X_C - X_C)^2}$$

$$28.28 = \sqrt{400 + X_C^2}$$

$$X_C = 19.6$$

$$X_C = 20$$

$$Z = 28.28$$

$$\frac{1}{\omega C} = X_C$$

$$C = \frac{1}{\omega X_C} = \frac{1}{1000 \times 20} = 5 \times 10^{-6}$$

$$= 50 \times 10^{-6}$$


$$= 50 \mu F$$


$$\omega L = X_L$$

$$L = \frac{X_L}{\omega} = \frac{40}{1000} = 0.04 H$$

Two circuits A & B are connected in parallel across a 200V, 50Hz mains. Circuit A consists of resistance of  $10\Omega$  and an inductance of  $0.12H$  connected in series with capacitor of  $40\mu F$ . Calculate

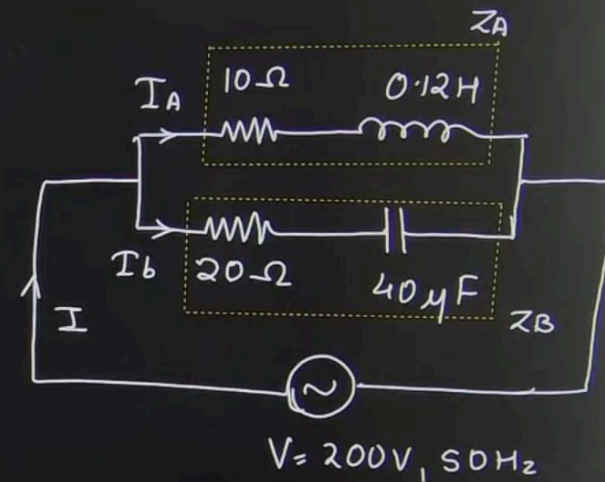- (i) Current in each branch
- (ii) Power factor
- (iii) Draw phasor diagram.



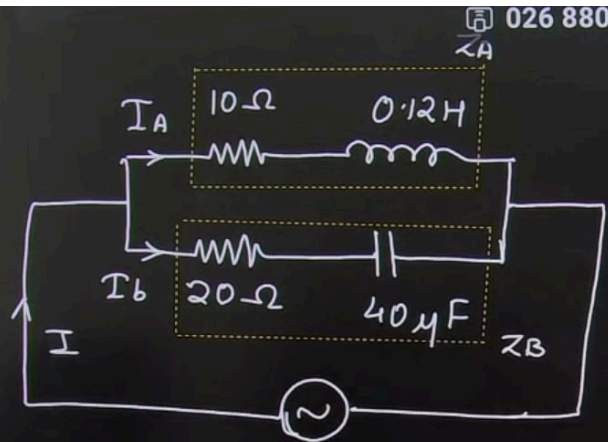

$$V = 200V, 50Hz$$

$$V = (200 \angle 0)$$

$$f = 50Hz$$

Consider circuit A.

$$\bar{Z}_A = R_A + jX_{LA}$$

$$\bar{Z}_A = 10 + j37.7 \Omega$$

$$\bar{Z}_A = (39, 75.14)$$

$$X_L = \omega \times L$$

$$= 2\pi \times f \times L$$

$$= 2\pi \times 50 \times 0.12$$

$$X_L = 37.699 \Omega$$

$$= 37.7 \Omega$$

Consider circuit B.

$$C = 40\mu F$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \times 50 \times 40 \times 10^{-6}}$$

$$= 79.57$$

$$X_C = 79.6 \Omega$$

$$Z_B = R_B - jX_C$$

$$\bar{Z}_B = 20 - j79.6 \Omega$$

$$\bar{Z}_B = (82.07, 2 - 75.896)$$



**Product -  
Rectangular/Complex  
form**

**Add/sub - Polar Form**

$$V = (200 \angle 0)$$

$$f = 50 \text{ Hz}$$

Consider circuit A.

$$\bar{Z}_A = R_A + jX_{LA}$$

$$\bar{Z}_A = 10 + j37.7 \Omega$$

$$\bar{Z}_A = (39, \angle 75.14)$$

$$X_L = \omega \times L$$

$$= 2\pi \times f \times L$$

$$= 2\pi \times 50 \times 0.12$$

$$X_L = 37.699 \Omega$$

$$= 37.7 \Omega$$

$$\angle B = (82.07, \angle -75.896)$$

$$\frac{1}{\bar{Z}} = \frac{1}{\bar{Z}_A} + \frac{1}{\bar{Z}_B}$$

$$\bar{Z} = \frac{\bar{Z}_B \cdot \bar{Z}_A}{\bar{Z}_A + \bar{Z}_B} = \frac{(82.07, \angle -75.896)}{(39, \angle 75.14)} \cdot (10 + j37.7) + (20 - j79.6)$$

$$= \frac{(82.07 \times 39, \angle -75.896 + 75.14)}{30 - j41.9}$$

$$= (3200.73 \angle -0.75)$$

$$= \frac{(3200.73 \angle -0.75 - (-54.39))}{51.53}$$

$$\bar{Z} = (62.01 \angle 53.63) \Omega$$

$$\bar{Z} = (36.77 + j49.93) \Omega$$

$$\begin{aligned}\bar{Z}_A &= R_A + jX_{LA} = 2 \times \pi \times 50 \times 0.12 \\ \bar{Z}_A &= 10 + j37.7 \Omega \quad X_L = 37.699 \Omega \\ \bar{Z}_A &= (39, \angle 75.14) = 37.7 \Omega.\end{aligned}$$

$$\phi = 53.63$$

$$I_A = \frac{V}{Z_A} = \left( \frac{200, \angle 0}{39, \angle 75.14} \right) = (5.128, \angle -75.14)$$

$$I_B = \frac{V}{Z_B} = \left( \frac{200 \angle 0}{82.07, \angle -75.896} \right) = (2.44, \angle 75.896)$$

$$\begin{aligned}\bar{Z} &= \frac{\bar{Z}_B \cdot \bar{Z}_A}{\bar{Z}_A + \bar{Z}_B} = \frac{(82.07, \angle -75.896)(39, \angle 75.14)}{(10 + j37.7) + (20 - j79.6)} \\ &= \frac{(82.07 \times 39, \angle -75.896 + 75.14)}{30 - j41.9} \\ &= \frac{(3200.73 \angle -0.75)}{(51.53 \angle -54.39)} \\ &= \left( \frac{3200.73}{51.53} \angle -0.75 - (-54.39) \right) \\ &= (62.01 \angle 53.63) \Omega \\ \bar{Z} &= (36.77 + j49.93) \Omega\end{aligned}$$

$$\begin{aligned}\bar{Z}_A &= R_A + jX_{LA} = 2 \times \pi \times 50 \times 0.12 \\ \bar{Z}_A &= 10 + j37.7 \Omega \quad X_L = 37.699 \Omega \\ \bar{Z}_A &= (39, \angle 75.14) = 37.7 \Omega.\end{aligned}$$

$$\phi = 53.63 \quad pf = \cos \phi = \cos 53.63 = 0.594$$

$$I_A = \frac{V}{Z_A} = \left( \frac{200, \angle 0}{39, \angle 75.14} \right) = 0.6 \text{ [lagging]} = (5.128, \angle -75.14)$$

$$I_B = \frac{V}{Z_B} = \left( \frac{200 \angle 0}{82.07, \angle -75.896} \right) = (2.44, \angle 75.896)$$

$$\begin{aligned}\bar{Z} &= \frac{\bar{Z}_B \cdot \bar{Z}_A}{\bar{Z}_A + \bar{Z}_B} = \frac{(82.07, \angle -75.896)(39, \angle 75.14)}{(10 + j37.7) + (20 - j79.6)} \\ &= \frac{(82.07 \times 39, \angle -75.896 + 75.14)}{30 - j41.9}\end{aligned}$$

$$= (3200.73, \angle -0.75)$$

$$= (51.53, \angle -54.39) \left( \frac{3200.73, \angle -0.75 - (-54.39)}{51.53} \right)$$

$$\bar{Z} = (62.01, \angle 53.63) \Omega$$

$$\bar{Z} = (36.77 + j49.93) \Omega$$



$$I_A = \frac{V}{Z_A} = \left( \frac{200 \angle 289.024}{39 \angle 75.14} \right) = \underline{\underline{0.6 \text{ [lagging]}}} \quad (51.53 \angle -54.39)$$

$$= (5.128 \angle -75.14)$$

$$I_B = \frac{V}{Z_B} = \left( \frac{200 \angle 0}{82.07 \angle -75.896} \right)$$


$$= (2.44 \angle 75.896)$$

$$\bar{Z} = (62.01 \angle 53.63) \Omega$$

$$\bar{Z} = (36.77 + j 49.93) \Omega$$

$$I = \frac{V}{\bar{Z}} = \frac{200 \angle 0}{(62.01 \angle 53.63)}$$
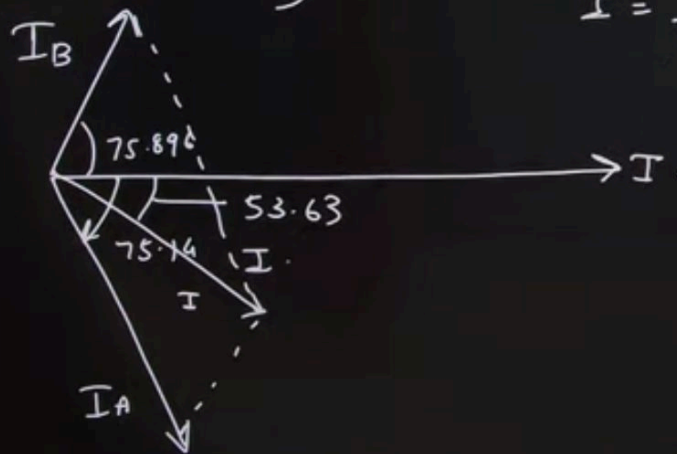
$$= \underline{\underline{3.22 \angle -53.63}}$$




Determine the equivalent impedance  $Z$  of circuit shown in figure

$$Z = R + j(X_L - X_C)$$

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

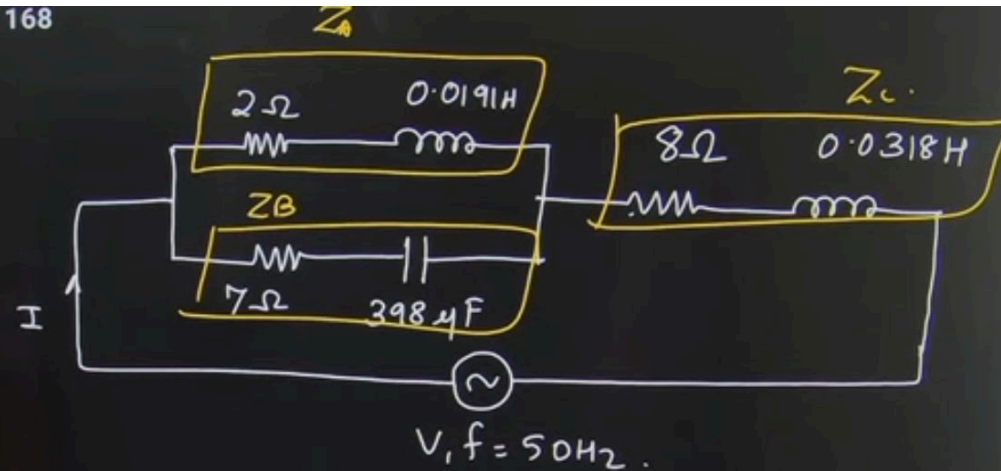
$$Z = R + j\left(2\pi fL - \frac{1}{2\pi fC}\right)$$



Determine the equivalent impedance  $\bar{Z}$  of circuit shown in figure

$$\begin{aligned} Z &= R + j(X_L - X_C) \\ Z &= R + j(\omega L - \frac{1}{\omega C}) \\ Z &= R + j(2\pi fL - \frac{1}{2\pi fC}) \end{aligned}$$

$$\begin{aligned} Z_A &= R + j(2\pi fL - \frac{1}{2\pi fC}) \\ &= 2 + j(2\pi f 0.0191) \\ \bar{Z}_A &= 2 + j(6) \Omega \\ &= (6.32 \angle 71.56) \end{aligned} \quad \left| \quad \begin{aligned} Z_B &= 7 + j(0 - \frac{1}{2\pi \times 50 \times 398 \times 10^{-6}}) \\ \bar{Z}_B &= 7 - j(8) \Omega = (10.63 \angle -48.81) \\ Z_C &= 8 + j(2\pi \times 50 \times 0.0318) \\ \bar{Z}_C &= 8 + j10 = (12.806 \angle 51.34) \end{aligned}$$

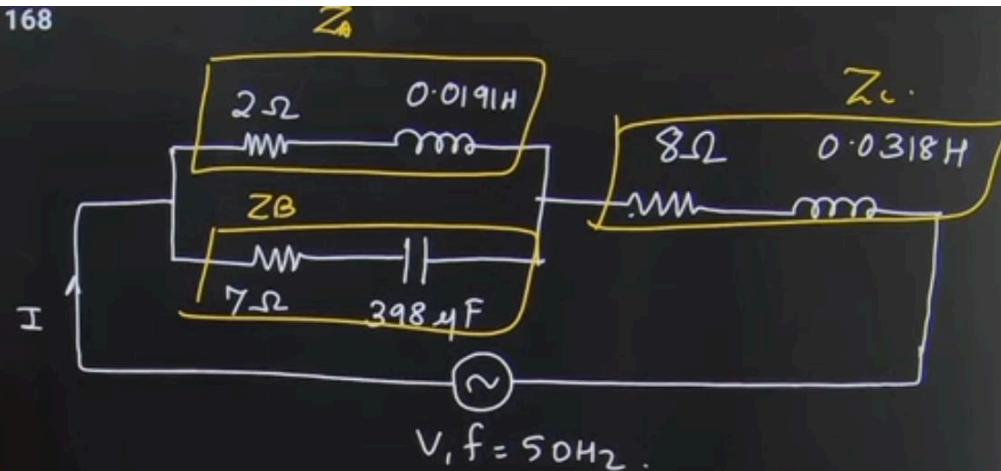

Total Impedance  $Z = \overset{026\ 880}{Z_A || Z_B} + Z_C$

$$Z = \frac{Z_B \cdot Z_A}{Z_A + Z_B} + Z_C$$

$$= \frac{(10 \angle 63^\circ)(6 \angle -71.56^\circ)}{(2 + j6) + (7 - j8)} + 8 + j10$$

$$= \frac{(10 \cdot 6)(\angle -8.56^\circ)}{(9 - 2j)} + 8 + j10$$

$$\boxed{Z = 13.94 + j14.205} = \frac{67.18 \angle 22.76^\circ}{9.22 \angle 12.53^\circ} + 8 + j10$$

$$\underline{\underline{\bar{Z} = (13.9, \angle 45.53)}} = \left( \frac{67.18}{9.22} \angle 22.76^\circ + 12.53^\circ \right) + 8 + j10$$

$$= (7.28 \angle 35.29^\circ) + 8 + j10 = 5.94 + j4.205 + 8 + j10$$