

Admittance (Y)

It is defined as the reciprocal of Impedance ohm Ω

$$\text{Admittance, } Y = \frac{1}{Z} = \frac{I}{V}$$



Unit = mho, \mathcal{U}

$$Z = \frac{V}{I}$$

If Admittance \uparrow , current \uparrow

* Components of Admittance

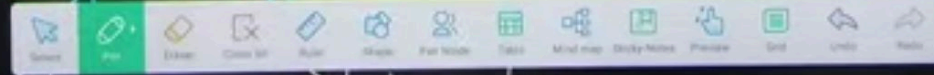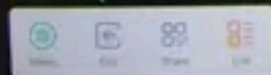' Admittance triangle is opposite to Impedance triangle.



Admittance (Y)

It is defined as the reciprocal of Impedance ohm Ω


$$\text{Admittance, } Y = \frac{1}{Z} = \frac{I}{V}$$











Unit = mho, \mathcal{U}

If Admittance \uparrow , current \uparrow

* Components of Admittance


' Admittance triangle is opposite to Impedance triangle.
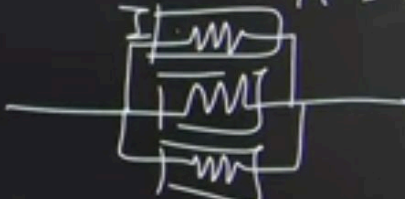
$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$
$$Z = \frac{V}{I}$$
$$Y_T = Y_1 + Y_2 + Y_3$$

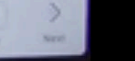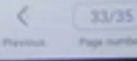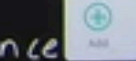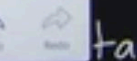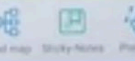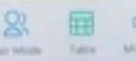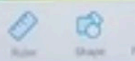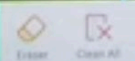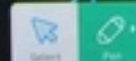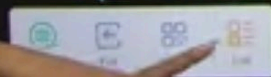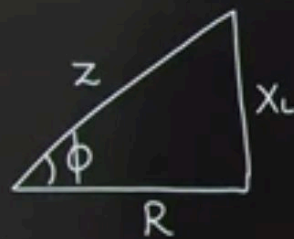
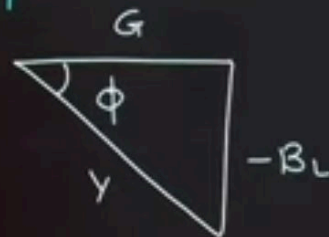


* Components of Admittance

Admittance triangle is opposite to Impedance triangle.



Impedance



Admittance

G = conductance

$$G = Y \cos \phi = \frac{R}{Z^2}$$

 B_L - Susceptance

$$B_L = Y \sin \phi = \frac{X_L}{Z_L}$$


$$Y \cos \phi$$

$$\frac{1}{2} \times \frac{R}{2}$$


$$\frac{k}{z^2}$$

In admittance the angle becomes -ve.

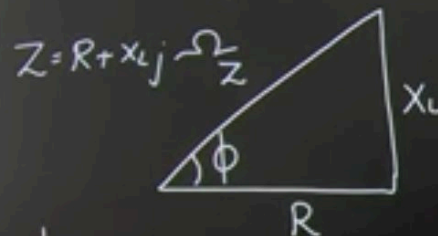Admittance triangle is opposite to Impedance triangle.



Impedance

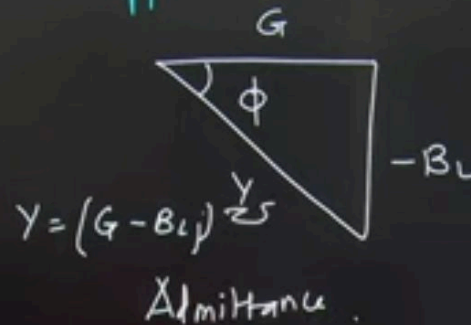

$G = \text{conductance}$



$$G = Y \cos \phi = \frac{R}{Z^2}$$

$B_L = \text{Susceptance}$

$$B_L = Y \sin \phi = \frac{X_L}{Z^2}$$

$$\frac{1}{Z} \times \frac{R}{Z} = \frac{R}{Z^2}$$

In admittance the angle becomes -ve.

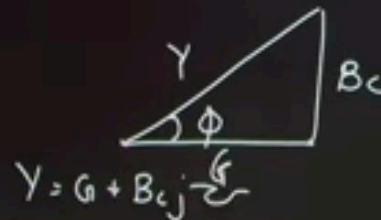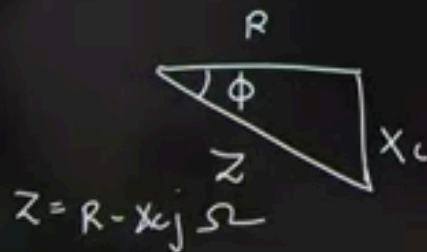


Q. Three loads are placed across 230V, 50Hz supply. The loads are $(10 \angle -30) \Omega$, $(20 \angle 60) \Omega$ and $(40 \angle 0) \Omega$.

Find i) Admittance (Y) ii) Equivalent Impedance iii) Power consumed & iv) power factor

$$Z_1 = 10 \angle -30 \Omega = 8.66 - 5j \Omega$$

$$Z_2 = 20 \angle 60 \Omega = 10 + 17.32j \Omega$$

$$Z_3 = 40 \angle 0 \Omega = 40 \Omega$$

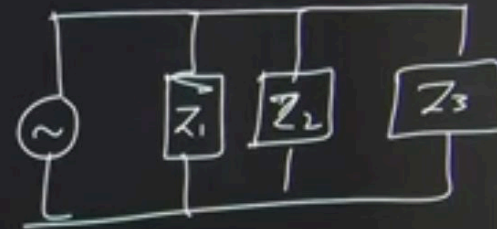

Q. Three loads are placed across 230V, 50Hz supply. The loads are $(10 \angle -30) \Omega$, $(20 \angle 60) \Omega$ and $(40 \angle 0) \Omega$.

Find i) Admittance (Y) ii) Equivalent Impedance iii) Power consumed & iv) power factor

$$Z_1 = 10 \angle -30 \Omega = 8.66 - 5j \Omega$$

$$Z_2 = 20 \angle 60 \Omega = 10 + 17.32j \Omega$$

$$Z_3 = 40 \angle 0 \Omega = 40 \Omega$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{10 \angle -30} = \frac{1 \angle 30}{10} = 0.1 \angle 30 = 0.086 + 0.05j$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{20 \angle 60} = 0.05 \angle -60 = 0.025 - 0.043j$$

$$Y_3 = \frac{1}{Z_3} = \frac{1}{40 \angle 0} = 0.025 \angle 0 = 0.025 + 0j$$

Total Admittance.

$$Y_T = Y_1 + Y_2 + Y_3$$

=

Q. Three loads are placed across 230V, 50Hz supply. The loads are $(10 \angle -30) \Omega$, $(20 \angle 60) \Omega$ and $(40 \angle 0) \Omega$.

Find i) Admittance (Y) ii) Equivalent Impedance iii) Power consumed & iv) power factor

$$10 \angle -30 \Omega = 8.66 - 5j \Omega$$

$$20 \angle 60 \Omega = 10 + 17.32j \Omega$$

$$40 \angle 0 \Omega = 40 \Omega$$

$$\frac{1}{Z_1} = \frac{1}{10 \angle -30} = \frac{1}{10} \angle 30 = 0.1 \angle 30 = 0.086 + 0.05j$$

$$\frac{1}{Z_2} = \frac{1}{20 \angle 60} = 0.05 \angle -60 = 0.025 - 0.043j$$

$$\frac{1}{Z_3} = \frac{1}{40 \angle 0} = 0.025 \angle 0 = 0.025 + 0j$$

Total Admittance.

$$Y_T = Y_1 + Y_2 + Y_3$$

$$= 0.086 + 0.05j + 0.025 - 0.043j + 0.025$$

$$Y_T = 0.136 + 0.007j \quad 0.136 \angle 2.94$$

Equivalent Impedance Z

$$Z = \frac{1}{Y}$$

$$= \frac{1}{0.136 \angle 2.94} = \frac{7.35 \angle -2.94}{0.136} = 7.34 - 0.37j$$

Q. Three loads are placed across 230V, 50Hz supply. The loads are $(10 \angle -30) \Omega$, $(20 \angle 60) \Omega$ and $(40 \angle 0) \Omega$.

Find i) Admittance (Y) ii) Equivalent Impedance iii) Power consumed & iv) power factor

$$P = VI \cos \phi$$

$$= 230 \times 31.35 \times \cos(-2.94)$$

$$= 7201 \text{ W}$$

$$= \underline{\underline{7.2 \text{ kW}}}$$

$$I = \frac{V}{Z}$$

$$= \frac{230 \angle 0}{7.34 \angle -2.94}$$

$$= 31.35 \angle 2.94$$

Total Admittance.

$$Y_T = Y_1 + Y_2 + Y_3$$

$$= 0.086 + 0.05j + 0.025 - 0.043j + 1$$

$$Y_T = 0.136 + 0.007j$$

Equivalent Impedance Z

$$Z = \frac{1}{Y}$$

$$= \frac{1}{0.136 \angle 2.94} = \frac{7.35 \angle -2.94}{0.136} = 7.34 \angle -0.37j$$

Q. Three loads are placed across 230V, 50Hz supply. The loads are $(10 \angle -30) \Omega$, $(20 \angle 60) \Omega$ and $(40 \angle 0) \Omega$.

Find i) Admittance (Y) ii) Equivalent Impedance iii) Power consumed & iv) power factor

$$P = VI \cos \phi$$

$$= 230 \times 31.35 \times \cos(-2.94)$$

$$= 7201 \text{ W}$$

$$= \underline{\underline{7.2 \text{ kW}}}$$

$$\text{Power factor} = \cos \phi = \cos(-2.94)$$

$$= 0.99 = 1 // \text{ leading}$$

$$I = \frac{V}{Z}$$

$$= \frac{230 \angle 0}{7.34 \angle -2.94}$$

$$= 31.35 \angle 2.94$$

Total Admittance.

$$Y_T = Y_1 + Y_2 + Y_3$$

$$= 0.086 + 0.05j + 0.025 - 0.043j + 1$$

$$Y_T = 0.136 + 0.007j$$

Equivalent Impedance Z

$$Z = \frac{1}{Y}$$

$$= \frac{1}{0.136 \angle 2.94} = \frac{7.35 \angle -2.94}{0.136} = 7.34 - 0.37j$$

Q. Draw the admittance triangle between the terminals A & B labelling its sides with appropriate value & units in case of.

1) $X_L = 4 \Omega$, $X_C = 8 \Omega$, $R = 1 \Omega$

2) $X_L = 10 \Omega$, $X_C = 5 \Omega$, $R = 1 \Omega$


Case 1
 $Z_1 = 1 + 0j = (1 \angle 0) \Omega$

$Z_2 = 0 + 4j = (4 \angle 90) \Omega$

$Z_3 = 0 - 8j = (8 \angle -90) \Omega$

Total impedance
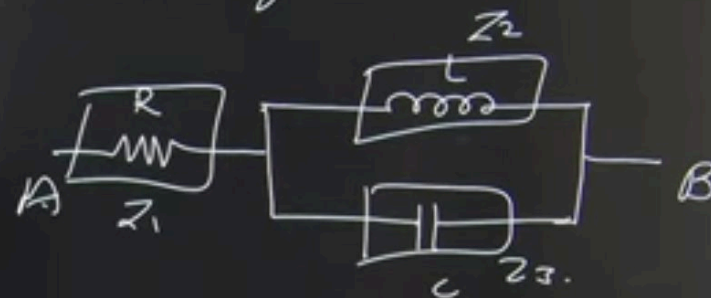
$$Z_T = Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3}$$



Q. Draw the admittance triangle between the terminals A & B labelling its sides with appropriate value & units in case of.

1) $X_L = 4 \Omega$, $X_C = 8 \Omega$, $R = 1 \Omega$

2) $X_L = 10 \Omega$, $X_C = 5 \Omega$, $R = 1 \Omega$

Case 1


$$Z_1 = 1 + 0j = (1 \angle 0) \Omega$$

$$Z_2 = 0 + 4j = (4 \angle 90) \Omega$$

$$Z_3 = 0 - 8j = (8 \angle -90) \Omega$$

Total impedance
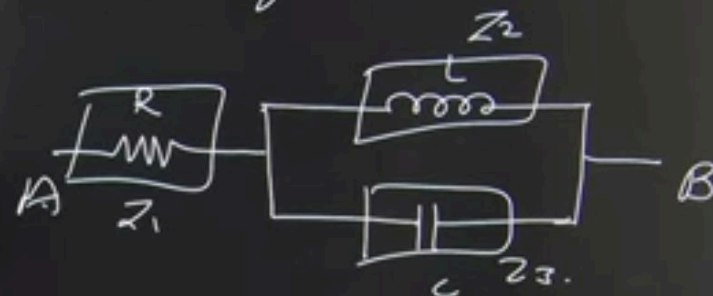
$$Z_T = Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3}$$



$$= 1 + 0j + \frac{(4 \angle 90)(8 \angle -90)}{0 + 4j + 0 - 8j}$$

$$= 1 + 0j + \frac{0 + 4j + 0 - 8j}{32 \angle 0}$$

$$= 1 + 0j + (8 \angle 90)$$

$$= 1 + 0j + 0 + 8j = 1 + 8j$$

1) $X_L = 4 \Omega$, $X_C = 8 \Omega$, $R = 1 \Omega$
~~Case 1~~ $X_L = 10 \Omega$, $X_C = 5 \Omega$, $R = 1 \Omega$

Case 1
 $Z_1 = 1 + 0j = (1 \angle 0) \Omega$

$Z_2 = 0 + 4j = (4 \angle 90) \Omega$


$Z_3 = 0 - 8j = (8 \angle -90) \Omega$

Total impedance

$Z_T = Z_1 + \frac{Z_2 \cdot Z_3}{Z_2 + Z_3}$

$Z_T = (1 + 8j) = (8.062 \angle 82.87) \Omega$

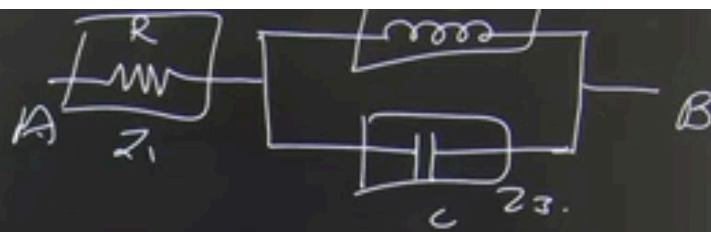$Y_T = \frac{1}{Z_T} = \frac{1}{(8.06 \angle 82.87)} = (0.124 \angle -82.87)$
 $= 0.0153 - 0.123j$



$= 1 + 0j + \frac{(4 \angle 90)(8 \angle -90)}{0 + 4j + 0 - 8j}$

$= 1 + 0j + \frac{0 + 4j + 0 - 8j}{32 \angle 0}$

$= 1 + 0j + (8 \angle 90)$

$= 1 + 0j + 0 + 8j = \boxed{1 + 8j}$

$$Z_T = Z_1 + \frac{Z_2 \cdot Z_3}{Z_2 + Z_3}$$

$$= 1 + 0j + (8 \angle 90^\circ)$$


$$= 1 + 0j + 0 + 8j = \boxed{1 + 8j}$$

$$Z_T = (1 + 8j) = (8.062 \angle 82.87^\circ) \Omega$$

$$Y_T = \frac{1}{Z_T} = \frac{1}{(8.06 \angle 82.87^\circ)} = (0.124 \angle -82.87^\circ)$$

$$= 0.0153 - 0.123j \text{ S}$$

Here complex part is negative

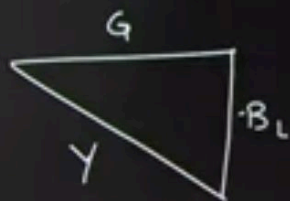

$$G = 0.0153 \text{ S}$$

$$B_L = -0.123 \text{ S}$$

$$Y = 0.124$$