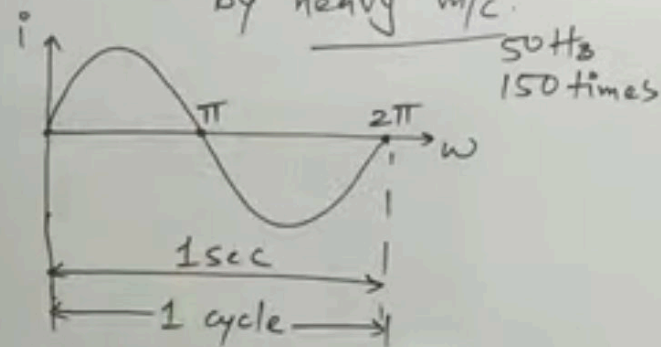


3 phase A.C. System (Circuits)

- ① Need of 3 ϕ Alternating Current.
- ② Generation
- ③ Wave form & phaser diagram.


3 phase A.C. System (Circuits)

① Need: When uninterrupted supply of current is required by heavy m/c.



3 phase A.C. System (Circuits)

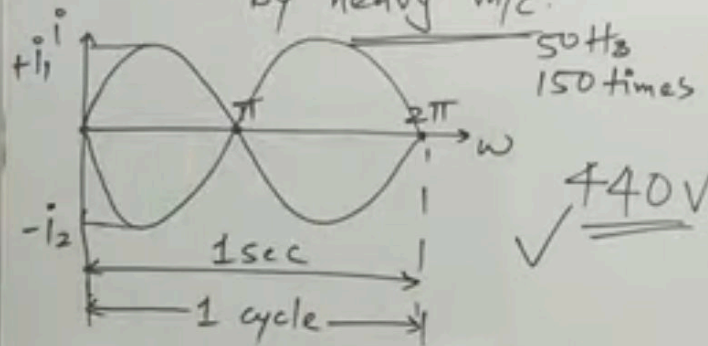① Need : When uninterrupted supply of current is required by heavy m/c.




$e = \text{emf}$

$N = \text{no. of turns}$

$d\phi/dt = \text{rate of change}$
 of magnetic flux




3 phase A.C. System (Circuits)

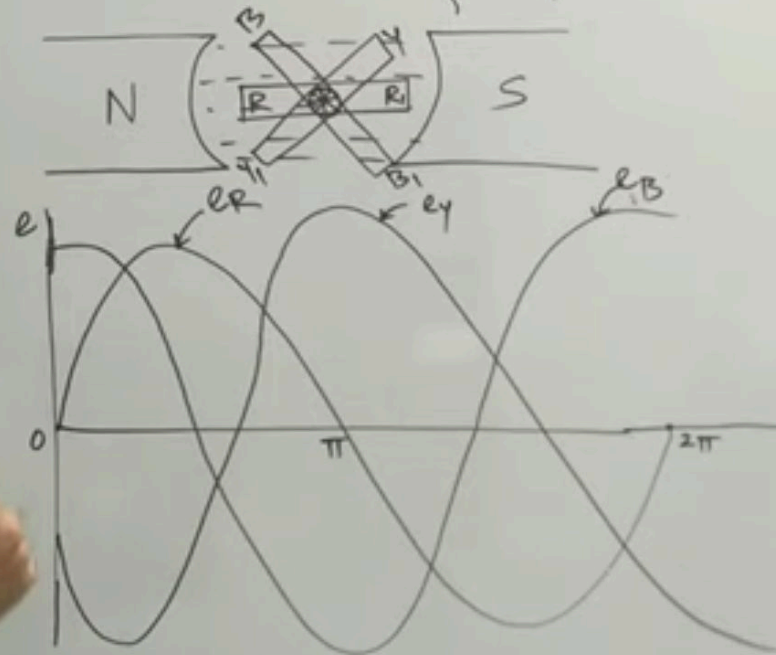② Generation $e = \ominus N \frac{d\phi}{dt}$ $E_Y = E_R = E_B$




3 phase A.C. System (Circuits)

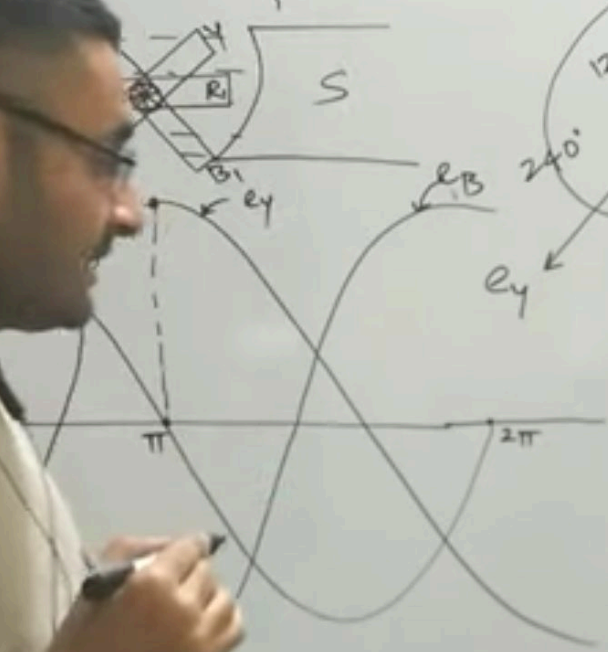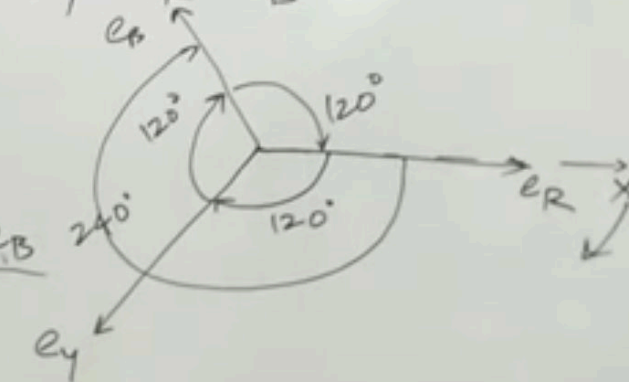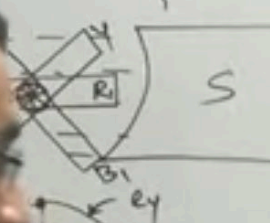② Generation $\mathcal{E} = \ominus N \frac{d\phi}{dt}$ $E_Y = E_R = E_B$




$$\begin{aligned} e_R &= E_R \sin \omega t \\ e_Y &= E_Y \sin(\omega t - 120^\circ) \\ e_B &= E_B \sin(\omega t - 240^\circ) \end{aligned}$$


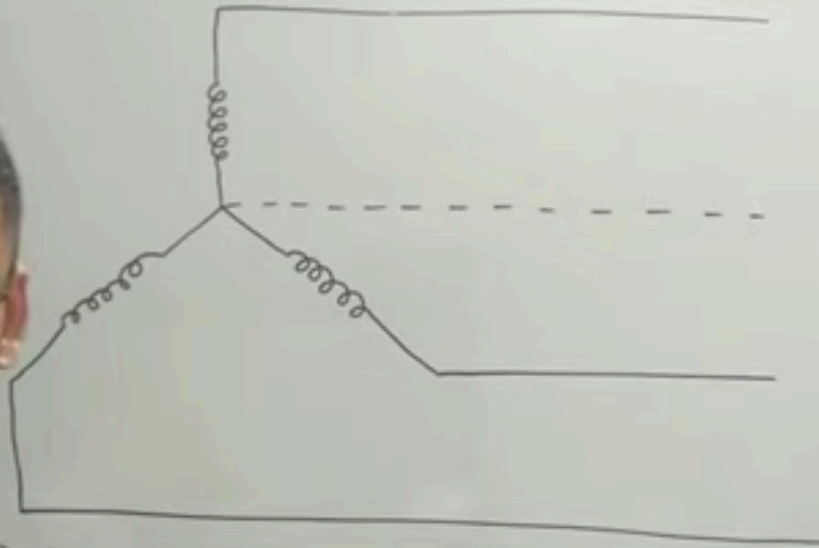
Important terms in Three phase AC circuit




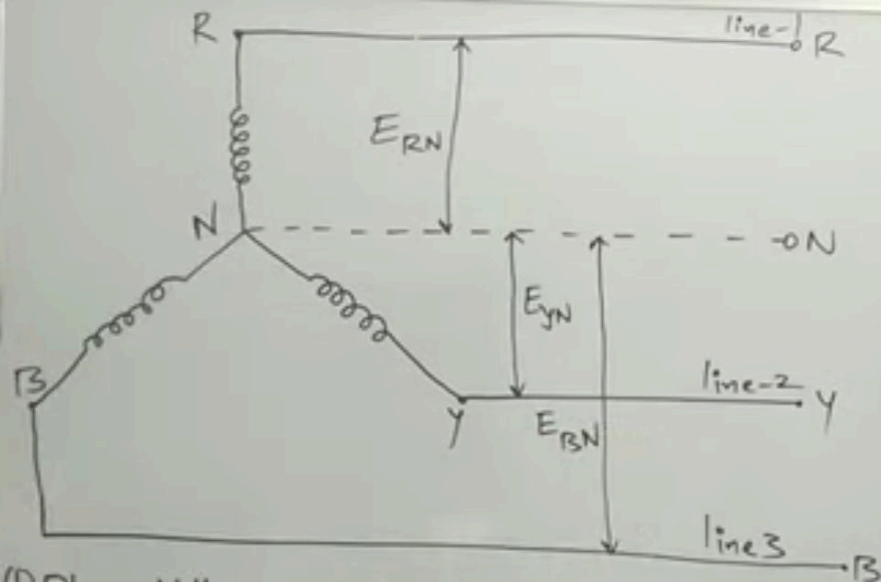
- ① Phase Voltage: "The voltage measured between line & neutral of supply" (E)
- ② Line Voltage: "The voltage measured between any two lines of supply" (V)
- ③ Phase Current: "Current flowing in each phase winding" (I_{ph})
- ④ Line Current: "Current flowing in each line" (I_L)



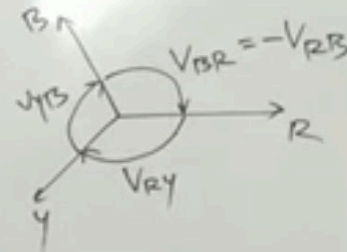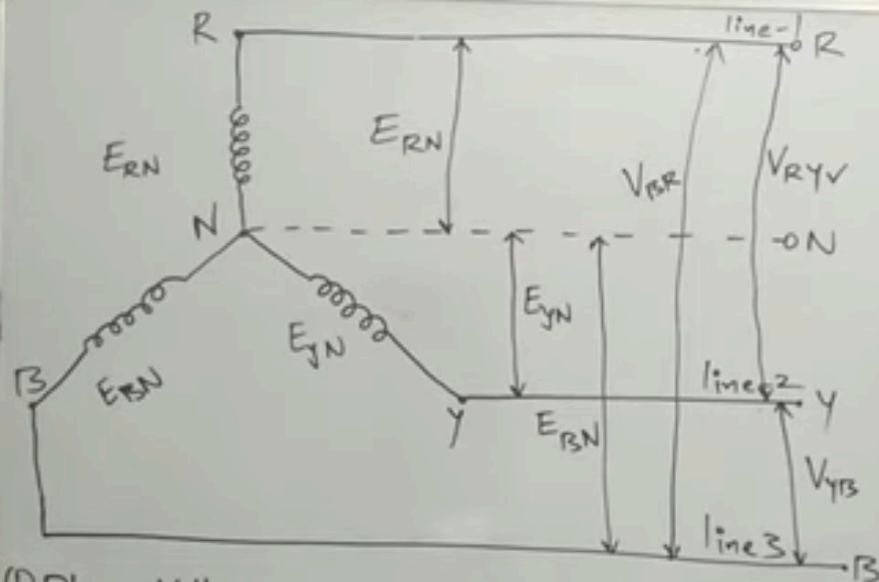- ① Phase Voltage: "The voltage measured between line & neutral of supply" (E)
- ② Line Voltage: "The voltage measured between any two lines of supply (V)"
- ③ Phase Current: "Current flowing in each phase winding" (I_{ph})
- ④ Line Current: "Current flowing in each line" (I_L)



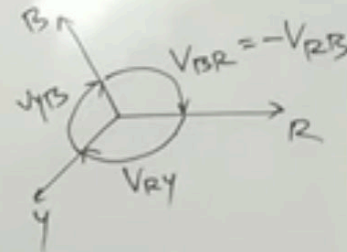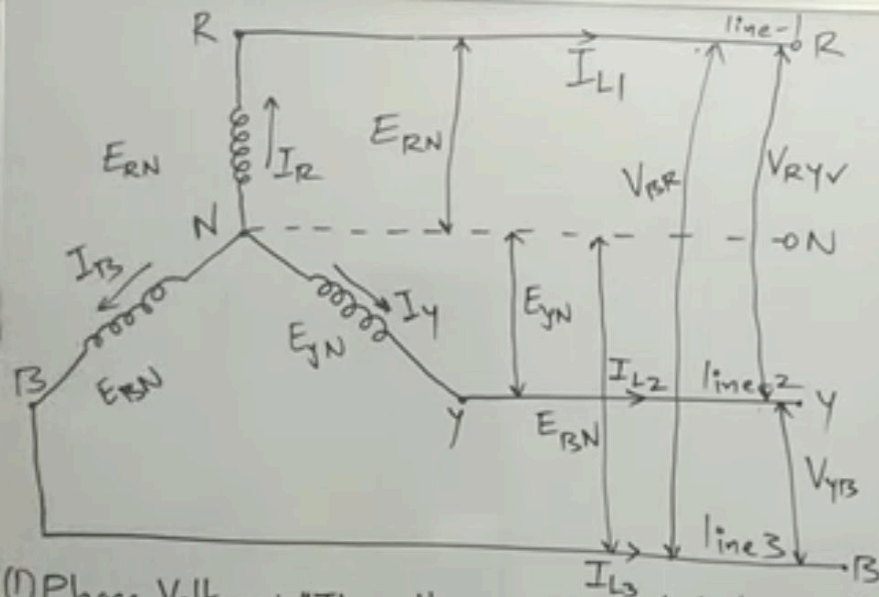- ① Phase Voltage: "The voltage measured between line & neutral of supply" (E)
- ② Line Voltage: "The voltage measured between any two lines of supply" (V)
- ③ Phase Current: "Current flowing in each phase winding" (I_{ph})
- ④ Line Current: "Current flowing in each line" (I_L)




- ① Phase Voltage: "The voltage measured between line & neutral of supply" (E)
- ② Line Voltage: "The voltage measured between any two lines of supply" (V)
- ③ Phase Current: "Current flowing in each phase winding" (I_{ph})
- ④ Line Current: "Current flowing in each line" (I_L)

⑤ Balanced system: It is one in which voltages in all phases are equal in magnitude ($e_R = e_Y = e_B$) and are displaced from one another by equal angles (120°). Also currents in these phases are equal in magnitude ($i_R = i_Y = i_B$) and are displaced by equal angle.

⑥ Balanced load: It is one in which the loads in all phases are equal in magnitude & having equal phases.

⑦ Unbalanced load: It is one in which the loads in all phases are different in magnitude & having different phase.

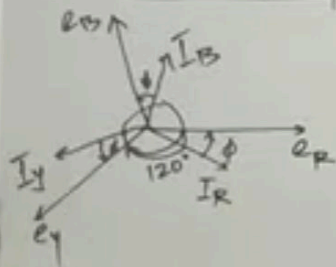⑤ Balanced system: It is one in which voltages in all phases are equal in magnitude ($e_R = e_Y = e_B$) and are displaced from one another by equal angles (120°). Also currents in these phases are equal in magnitude ($i_R = i_Y = i_B$) and are displaced by equal angle.



⑥ Balanced load: It is one in which the ^{120°} loads in all phases are equal in magnitude & having equal phases. ^{3φ motor}

⑦ Unbalanced load: It is one in which the ^{3φ motor} loads in all phases are different in magnitude & having different phase.

Three phase star
connection :

Line current phase
current

Line voltage phase
voltage

Power factor equation

⑧ 3 phase Star Connection (Phases diagram):

① $I_L = I_{ph}$

② $V_L = \sqrt{3} V_{ph}$

③ Power factor $= \sqrt{3} V_L I_L \cos \phi$

Three phase delta connection

3 phase Delta Connection (Phaser diagram):

① $V_L = V_{ph}$

② $I_L = \sqrt{3} I_{ph}$

③ Power factor = $\sqrt{3} V_L I_L \cos \phi$


Q) A balanced star connected load of $(4+j3)\Omega$ per phase is connected to a balanced 3 phase 400V supply. Find Line current, power factor, active power & Reactive power.

Solⁿ
=>




Q) A balanced star connected load of $(4+j3)\Omega$ per phase is connected to a balanced 3 phase 400V supply. Find Line current, power factor, active power & Reactive power.

Solⁿ
 $\Rightarrow (4+j3)\Omega$

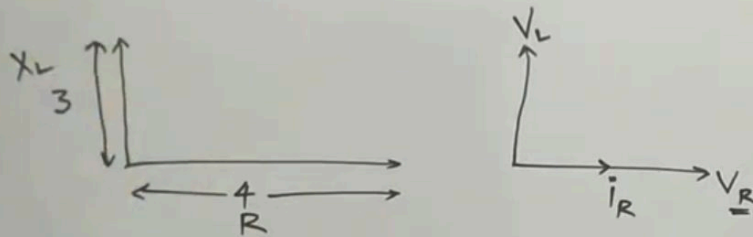

Q) A balanced star connected load of $(4+j3)\Omega$ per phase is connected to a balanced 3 phase 400V supply. Find Line current, power factor, active power & Reactive power.

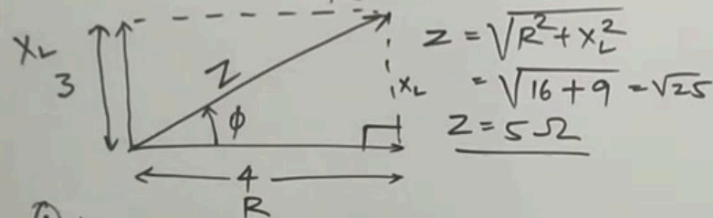Solⁿ
 $\Rightarrow (4+j3)\Omega$
 $X_L = 3\Omega$ $V_L = 400V$
 $R = 4\Omega$



① Line current (I_L)

$$I_L = I_{ph}$$

$$V_{ph} = I_{ph} Z$$

$$I_{ph} = \frac{V_{ph}}{Z} = \frac{230.94}{5}$$

$$V_L = \sqrt{3} V_{ph}$$


$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}}$$

$$V_{ph} = 230.94V$$

$$I_{ph} = 46.19A = I_L \quad \underline{\underline{Ans}}$$

Q) A balanced star connected load of $(4+j3)\Omega$ per phase is connected to a balanced 3 phase 400V supply. Find Line current, power factor, active power & Reactive power.

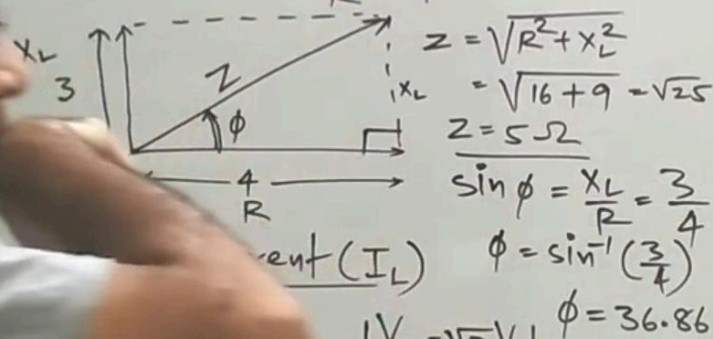Solⁿ
 $\Rightarrow (4+j3)\Omega$
 $X_L = 3\Omega$
 $R = 4\Omega$
 $V_L = 400V$



$$V_L = \sqrt{3} V_{ph}$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}}$$

$$V_{ph} = 230.94V$$

$$I_{ph} = \frac{V_{ph}}{Z} = \frac{230.94}{5}$$

$$I_{ph} = 46.19A = I_L \quad \underline{\text{Ans}}$$

② Power factor ($\cos \phi$)

$$\cos \phi = \frac{R}{Z} = \frac{4}{5}$$

$$\cos \phi = 0.8 \quad \underline{\text{Ans}}$$

③ Active Power (\cos) W

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 400 \times 46.19 \times 0.8$$

$$P = 25601.09W$$

$$P = 25.601kW \quad \underline{\text{Ans}}$$

④ Reactive (sin) VAR

$$P = \sqrt{3} V_L I_L \sin \phi$$

$$= \sqrt{3} \times 400 \times 46.19 \times \sin(36.86^\circ)$$

$$P = 19196.39VAR$$

$$P = 19.196kVAR \quad \underline{\text{Ans}}$$

Q) A delta connected balanced 3 phase load is supplied from 400V, 3 phase mains. The line current is 20A and Power taken by load is 10kW. Find,

(i) Impedance in each branch.

(ii) Power factor of load.

Soln
⇒

$$V_L = V_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

$$V_L = 400V = V_{ph}$$

$$I_L = 20A$$

$$I_{ph} = \frac{I_L}{\sqrt{3}} = \frac{20}{\sqrt{3}}$$

$$I_{ph} = 11.55A$$

$$P = 10kW$$
$$= 10 \times 10^3 W$$

Q) A delta connected balanced 3 phase load is supplied from 400 V, 3 phase mains. The line current is 20 A and Power taken by load is 10 kW. Find,

(i) Impedance in each branch.

(ii) Power factor of load.

Solⁿ

⇒ (i) Z

$$V = I R$$

$$V_{ph} = I_{ph} Z$$

$$Z = \frac{V_{ph}}{I_{ph}} = \frac{400}{11.55}$$

$$\boxed{Z = 34.63 \Omega} \text{ Ans}$$

$$V_L = V_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

$$V_L = 400 V = V_{ph}$$

$$I_L = 20 A$$

$$I_{ph} = \frac{I_L}{\sqrt{3}} = \frac{20}{\sqrt{3}}$$

$$I_{ph} = 11.55 A$$

$$P = 10 \text{ kW} \\ = 10 \times 10^3 \text{ W}$$

Q) A delta connected balanced 3 phase load is supplied from 400 V, 3 phase mains. The line current is 20 A and Power taken by load is 10 kW. Find,

(i) Impedance in each branch.

(ii) Power factor of load.

Solⁿ

(i) Z

$$V = I R$$

$$V_{ph} = I_{ph} Z$$

$$Z = \frac{V_{ph}}{I_{ph}} = \frac{400}{11.55}$$

$$Z = 34.63 \Omega \text{ Ans}$$

$$(ii) P = \sqrt{3} V_L I_L \cos \phi$$

$$\cos \phi = \frac{P}{\sqrt{3} V_L I_L}$$

$$\cos \phi = \frac{10 \times 10^3}{\sqrt{3} \times 400 \times 20}$$

$$V_L = V_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

$$V_L = 400 V = V_{ph}$$

$$I_L = 20 A$$

$$I_{ph} = \frac{I_L}{\sqrt{3}} = \frac{20}{\sqrt{3}}$$

$$I_{ph} = 11.55 A$$

$$\cos \phi = 0.7217$$

$$P = 10 \text{ kW} = 10 \times 10^3 \text{ W}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$