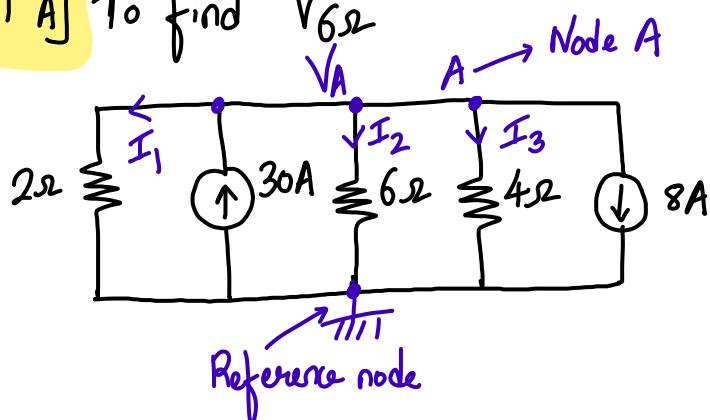


Q1 A] To find $V_{6\Omega}$



Using Nodal analysis,

KCL at node A,

$$8 + I_1 + I_2 + I_3 = 30$$

i.e $8 + \frac{V_A}{2} + \frac{V_A}{6} + \frac{V_A}{4} = 30$






i.e $0.5V_A + 0.16667V_A + 0.25V_A = 22$

i.e $0.91667V_A = 22$

i.e $V_A = 23.9999 V$

i.e $\boxed{V_A = 24 V}$


Q1 b) To find $R_{AB} = ?$

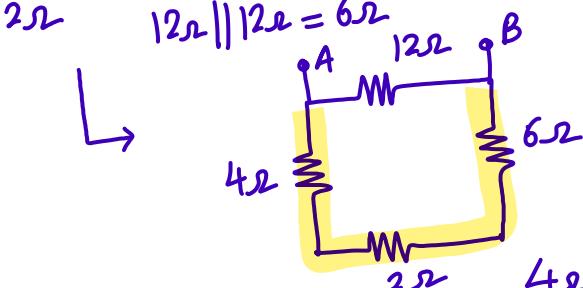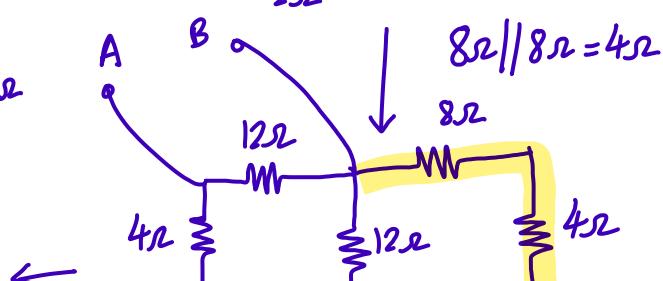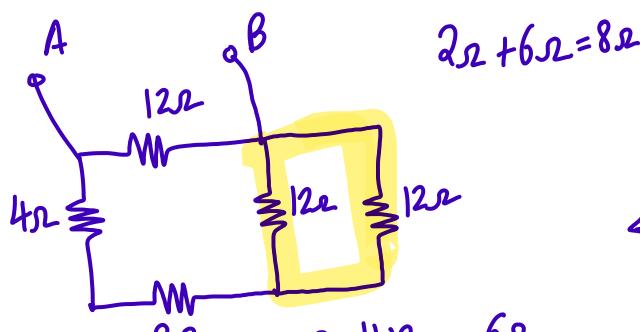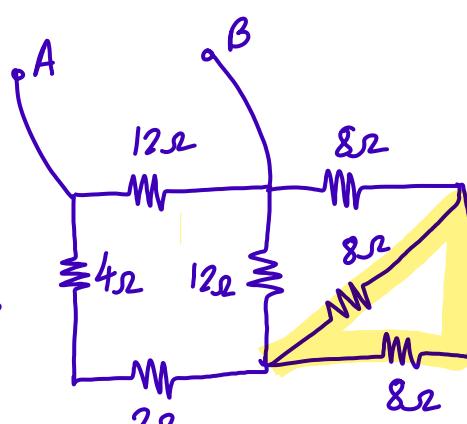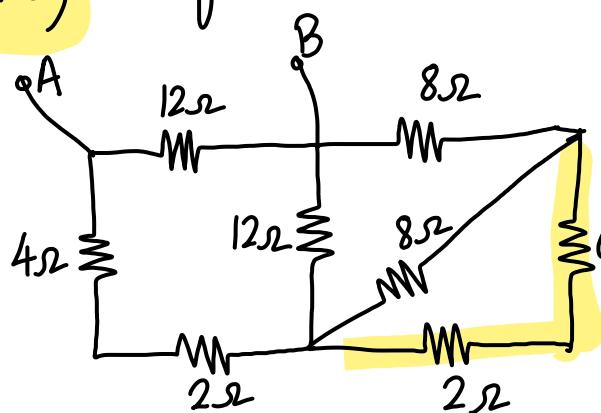

$4\Omega + 2\Omega + 6\Omega = 12\Omega$ $R_{AB} = 12\Omega // 12\Omega$

$\boxed{R_{AB} = 6\Omega}$

Q2. To find I_{152}

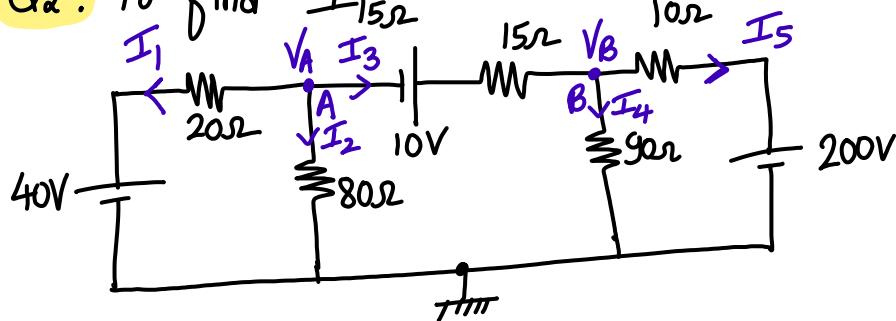

KCL at node A,

$$I_3 = I_4 + I_5$$

$$\frac{V_A + 10 - V_B}{15} = \frac{V_B}{90} + \frac{V_B - 200}{10}$$

$$\text{i.e. } 0.0667V_A + 0.6667 - 0.0667V_B = 0.01111V_B + 0.1V_B - 20$$

$$\text{i.e. } 0.0667V_A - 0.1778V_B = -20.6667 \quad \textcircled{2}$$

Solving $\textcircled{1}$ & $\textcircled{2}$, we get

$$\begin{bmatrix} 0.1292 & -0.0667 \\ 0.0667 & -0.1778 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 1.3333 \\ -20.6667 \end{bmatrix}$$

$$V_A = 87.218V$$


$$V_B = 148.95V$$

$$I_{152} = I_3 = \frac{V_A + 10 - V_B}{15} = \frac{87.218 + 10 - 148.95}{15}$$

$$\begin{aligned} I_{152} &= -3.4488 \text{ A} \rightarrow \\ I_{152} &= 3.4488 \text{ A} \leftarrow \end{aligned}$$

OR

Q2. To find I_{152} using mesh analysis

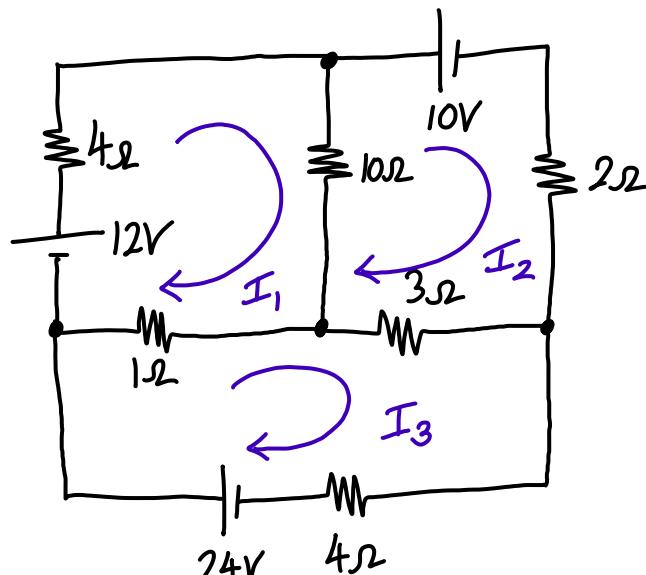

KVL to mesh 3,

$$24 - (I_3 - I_1) - 3(I_3 - I_2) - 4I_3 = 0$$

Using Nodal analysis,

KCL at node A,

$$I_1 + I_2 + I_3 = 0$$

$$\text{i.e. } \frac{V_A - 40}{20} + \frac{V_A}{80} + \frac{V_A + 10 - V_B}{15} = 0$$

$$\begin{aligned} \text{i.e. } 0.05V_A - 2 + 0.0125V_A + 0.0667V_A \\ + 0.6667 - 0.0667V_B = 0 \end{aligned}$$

$$\text{i.e. } 0.1292V_A - 0.0667V_B = 1.3333 \quad \textcircled{1}$$

$$KVL \text{ to mesh 1,} \\ 12 - 4I_1 - 10(I_1 - I_2) - (I_1 - I_3) = 0$$

$$\text{i.e. } -15I_1 + 10I_2 + I_3 = -12 \quad \textcircled{1}$$

KVL to mesh 2,

$$-10(I_2 - I_1) - 10 - 2I_2 - 3(I_2 - I_3) = 0$$

$$\text{i.e. } 10I_1 - 15I_2 + 3I_3 = 10 \quad \textcircled{2}$$

$$\text{i.e. } I_1 + 3I_2 - 8I_3 = -24 \quad \text{--- ③}$$

$$\begin{bmatrix} -15 & 10 & 1 \\ 10 & -15 & 3 \\ 1 & 3 & -8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -12 \\ 10 \\ -24 \end{bmatrix}$$

$$I_1 = \frac{791}{395} \text{ A}$$

$$I_2 = \frac{563}{395} \text{ A}$$

$$I_3 = \frac{299}{79} \text{ A}$$

$$I_{12} = I_1 - I_3 = \frac{791}{395} - \frac{299}{79}$$

$$I_{12} = -1.782 \text{ A} \quad \leftarrow$$

$$I_{12} = 1.782 \text{ A} \quad \rightarrow$$

[Q3 A] $v = 100 \sin(200\pi t)$

$$v = V_m \sin(\omega t + \phi)$$

i.e. $V_m = 100 \text{ V}$ — maximum voltage

$$V_{avg} = 0.637 V_m = 0.637 \times 100$$

$V_{avg} = 63.7 \text{ V}$ — Average voltage

$$V_{rms} = 0.707 V_m = 0.707 \times 100$$

$V_{rms} = 70.7 \text{ V}$ — RMS voltage


$$\omega = 2\pi f$$

$$\text{i.e. } 200\pi = 2\pi f \rightarrow f = 100 \text{ Hz}$$

$$T = \frac{1}{f} = \frac{1}{100} = 10 \text{ msec}$$

$$t_{diff} = \frac{T}{4} = \frac{10 \text{ ms}}{4} = 2.5 \text{ ms}$$

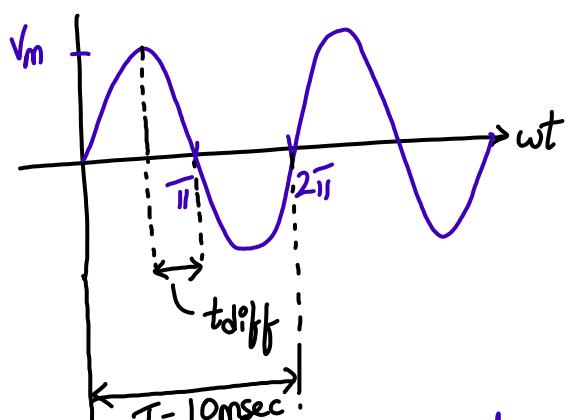
time difference between maximum value & next zero value



OR


(Q2A)] $v = V_m \sin \omega t$

i) Phasor diagram of pure resistor R

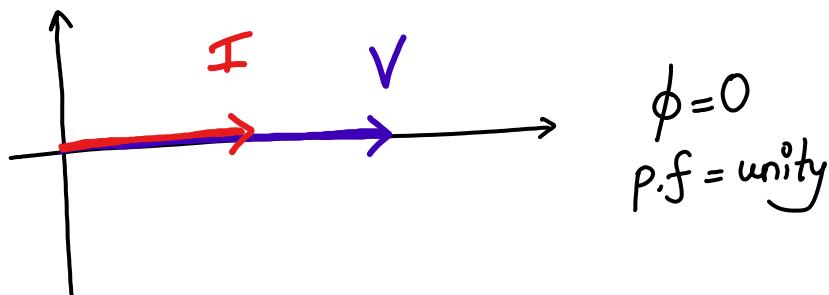


Taking voltage V as reference

Phasor diagram of pure inductor L

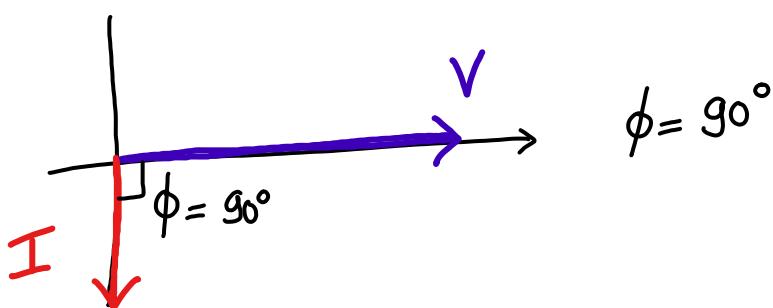


Taking voltage V as reference

Phasor diagram of pure capacitor C

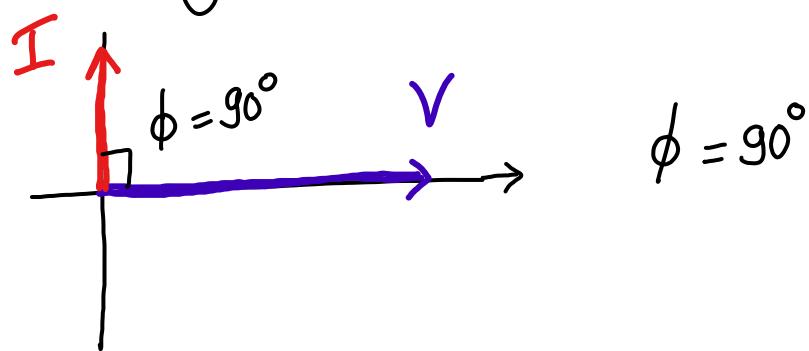


Taking voltage V as reference

Phasor diagram of RL series

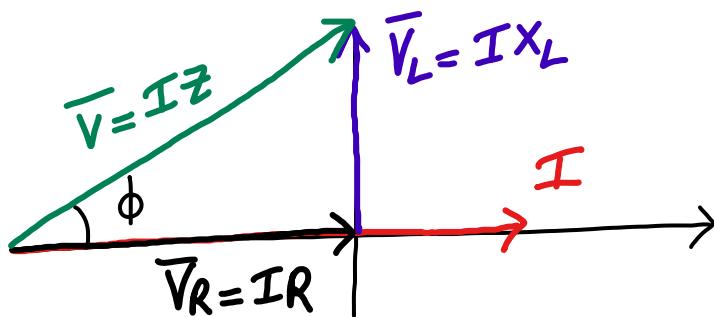


Taking current I as reference

Phasor diagram of RC series

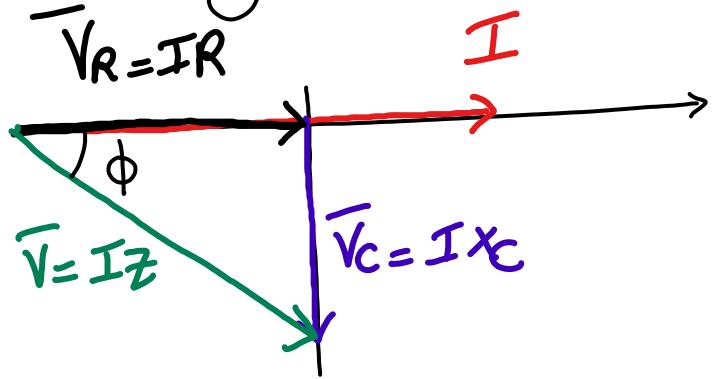


Taking current I as reference

Phasor diagram of RLC series

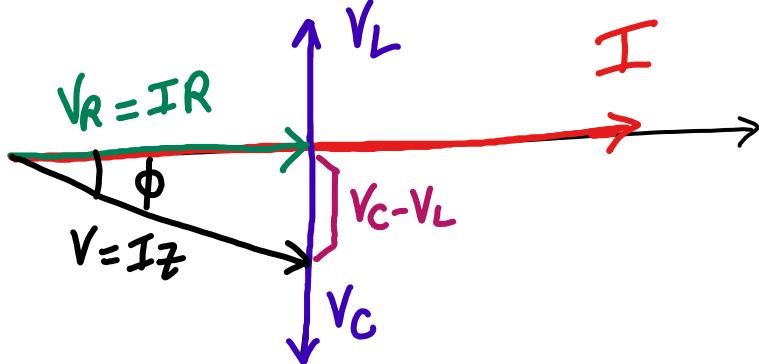

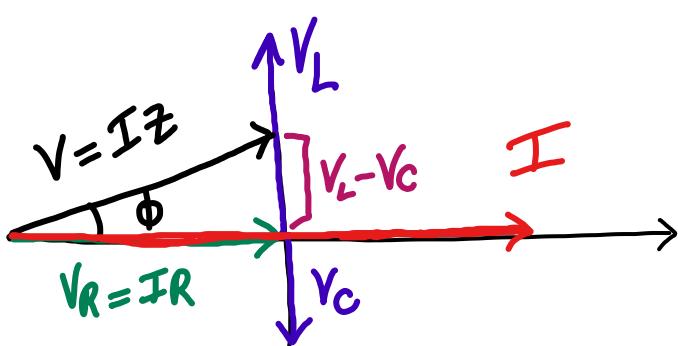Taking current I as reference
($X_C > X_L$)



Taking current I as reference
($X_L > X_C$)

Q3B) Given: $R = 5\Omega$, $L = 0.05H$, $V_{rms} = 230V$, $f = 50Hz$


To find: Z_{coil} , I , p.f

Solution: i) $Z_{coil} = R + jX_L$

$$ii) X_L = 2\pi fL = 2\pi \times 50 \times 0.05$$

$$X_L = 15.7079\Omega$$
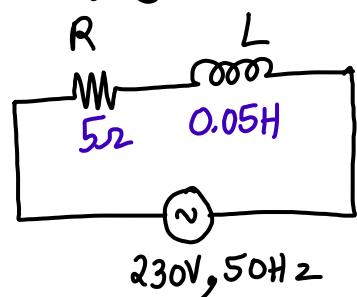
$$\text{i.e } Z_{coil} = 5 + j15.7079\Omega \rightarrow \text{Rectangular form}$$



$$iii) Z_{coil} = 16.4845 \angle 72.34^\circ \Omega \rightarrow \text{Polar form}$$

$$iv) I = \frac{V}{Z_{coil}} = \frac{230 \angle 0^\circ}{16.4845 \angle 72.34^\circ}$$

$$I = 13.9525 \angle -72.34^\circ A$$

$$v) p.f = \cos \phi = \cos(72.34^\circ)$$

$$p.f = 0.3034 \text{ lagging}$$

