

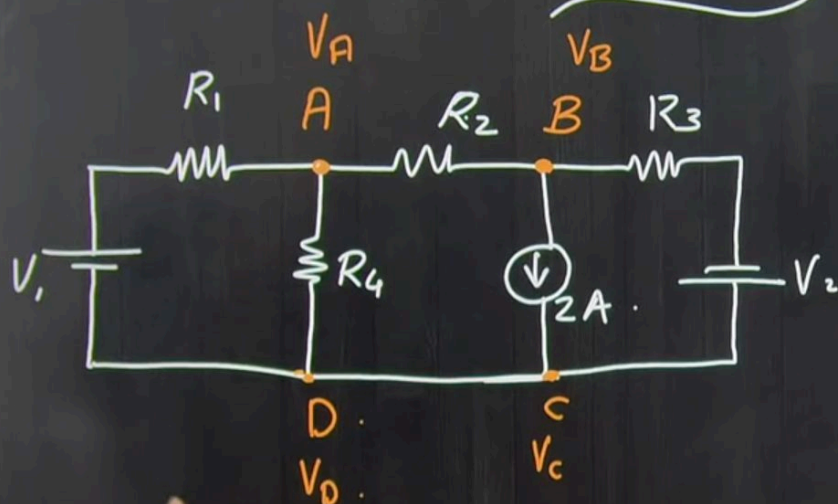


# Nodal analysis:

① Identify nodes.

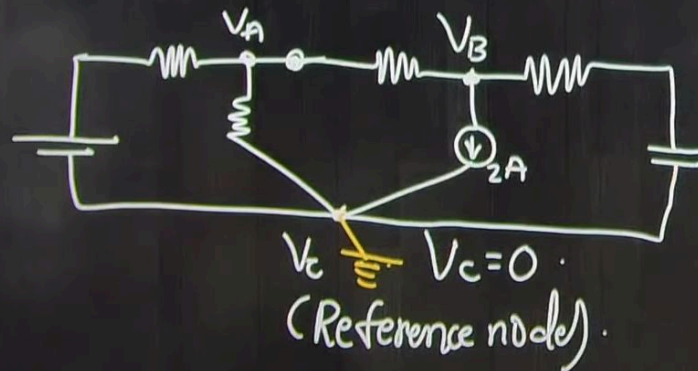

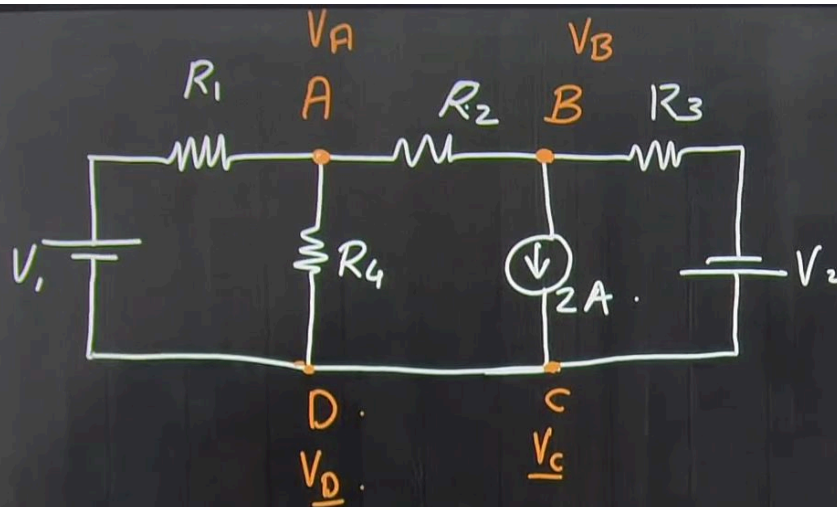

① Identify nodes.


② Reference node

Datum node.

Zero potential

③ Nodes naming.


07:40

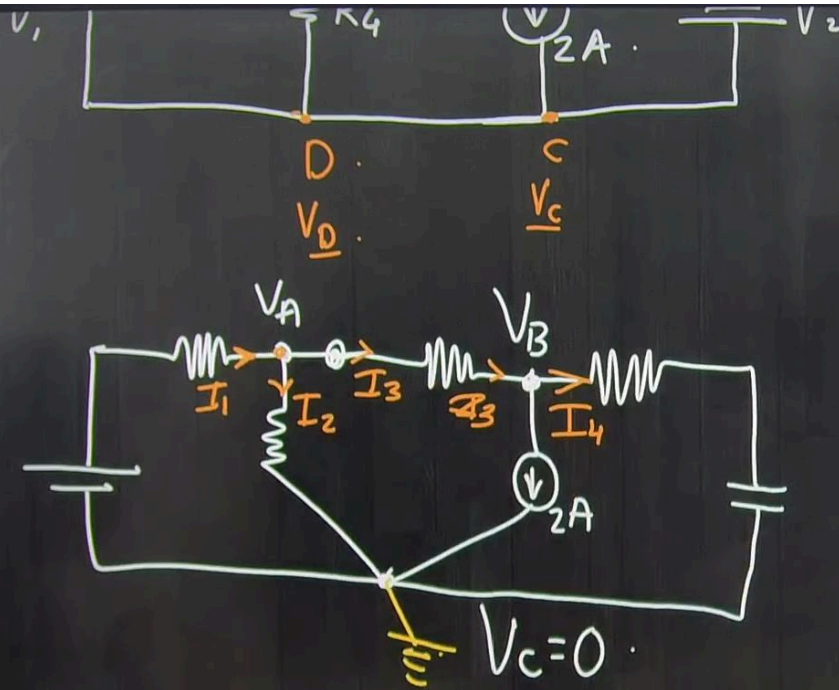

- Zero potential
- ③ Nodes naming.
  - ④ Branch currents & direction  $I_1, I_2, I_3, \dots$
  - ⑤  $I = \frac{V}{R}$ .
  - ⑥ Calculation of  $V_{//}$ .


find the current in various resistors of the circuit.

07:52

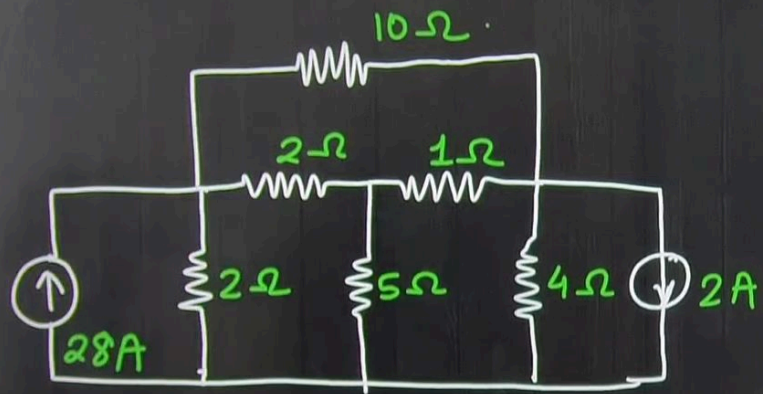




07:59

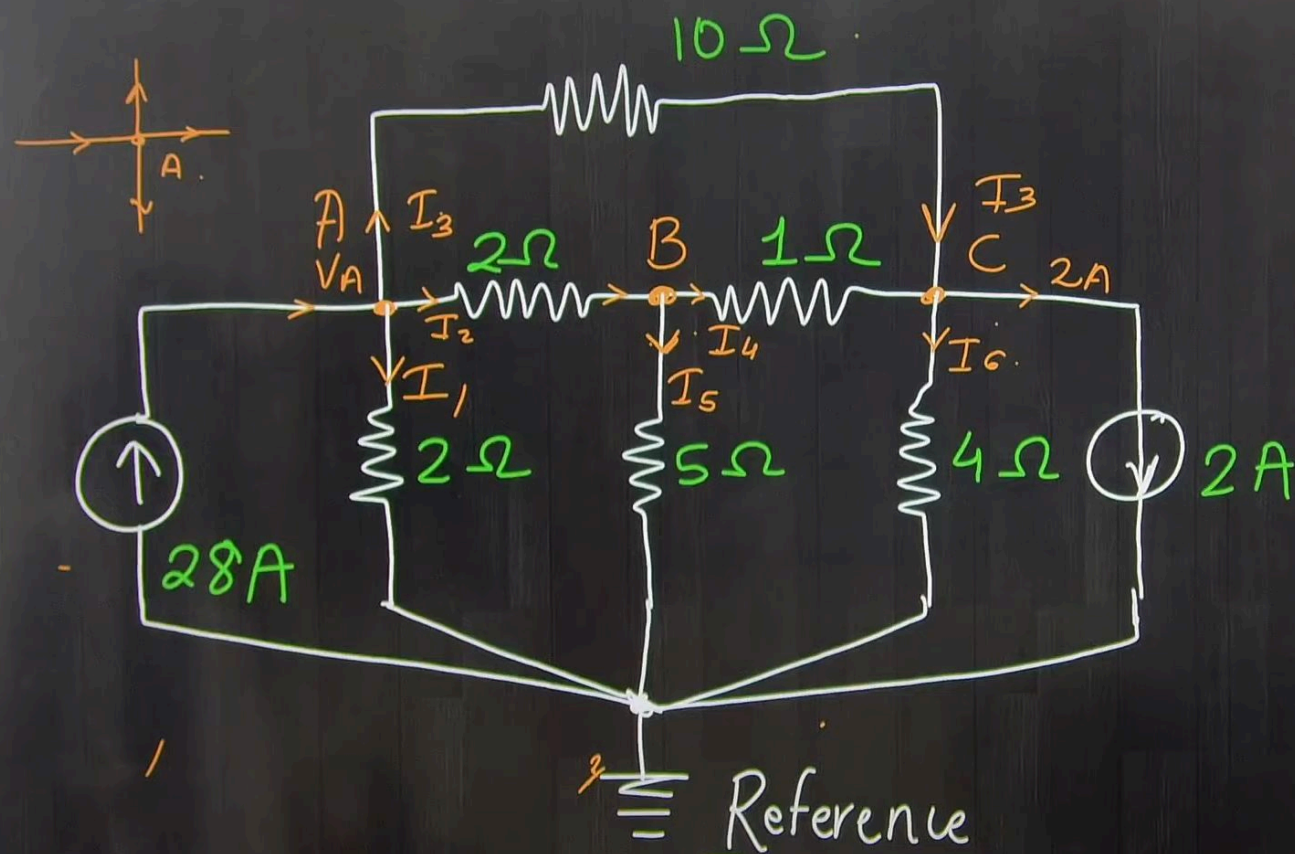

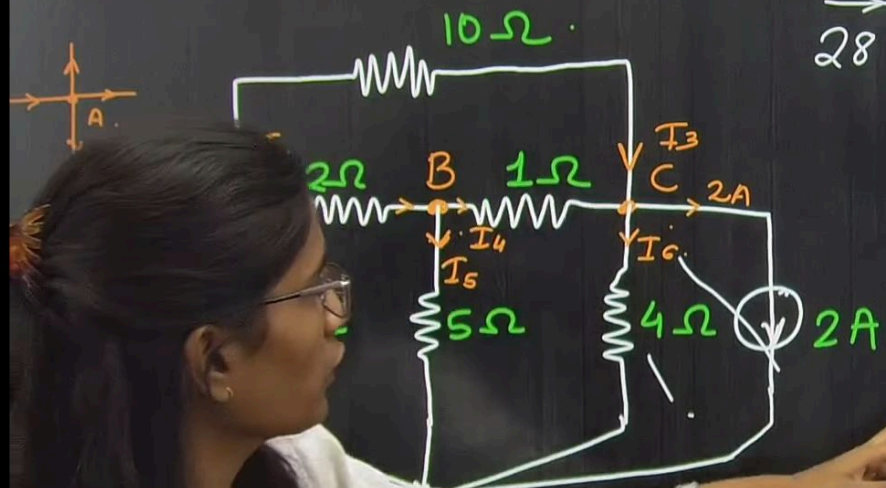
find the current in various resistors of the circuit.




Apply KCL at node A.

08:03

$$28 = I_1 + I_2 + I_3$$

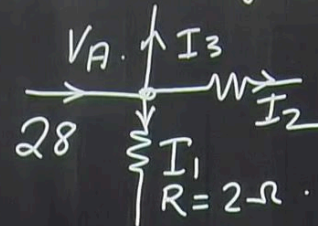

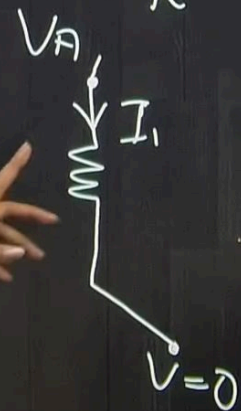
$$\frac{V}{R} \text{ at } I_1 = \frac{V_A - 0}{2}$$




node.

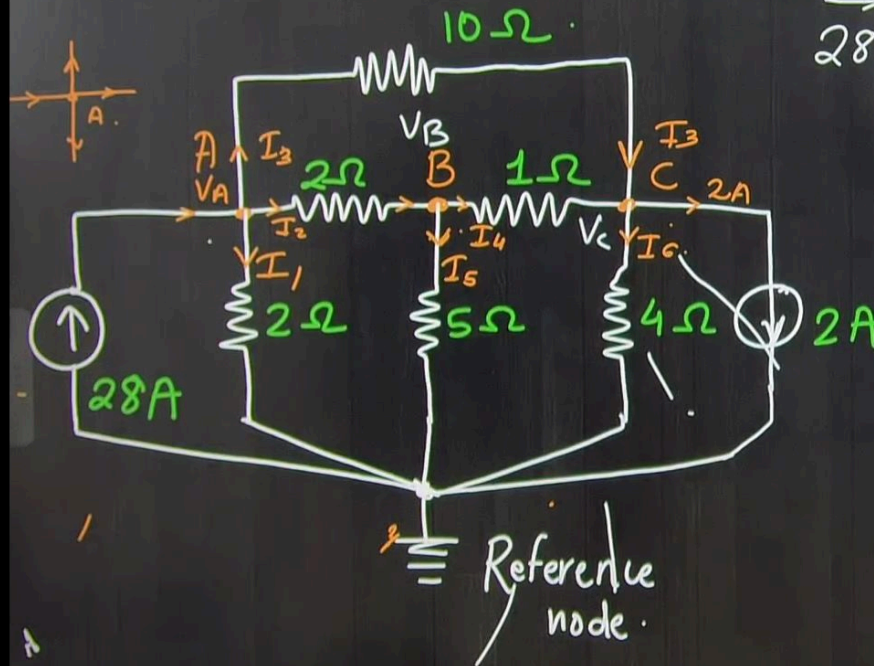find the current in various resistors of the circuit.



Apply KCL at node A.

08:05

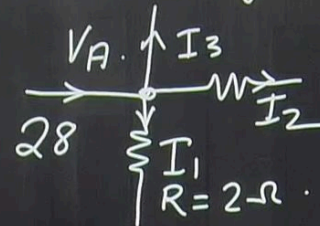


$$28 = I_1 + I_2 + I_3$$

$$\frac{V}{R} \text{ at}$$


$$I_1 = \frac{V_A - 0}{2}$$
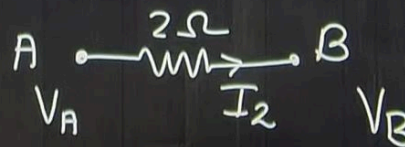
$$\frac{V}{R} \text{ at } I_2 = \frac{V_A - V_B}{2}$$






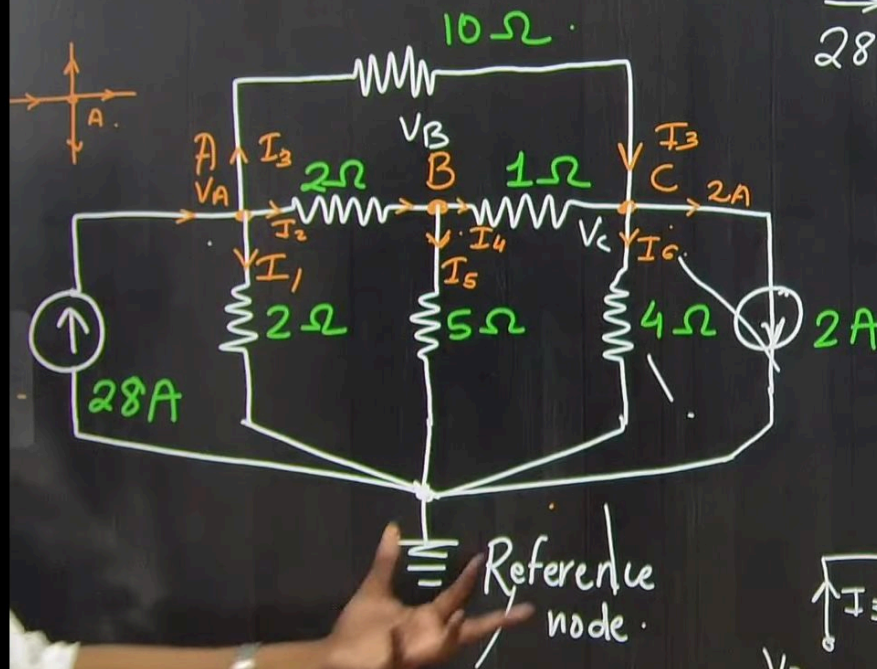find the current in various resistors of the circuit.



Apply KCL at node A.

08:07

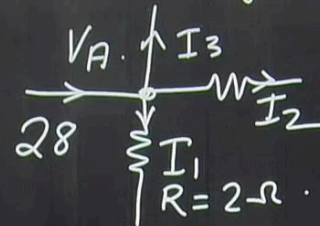


$$28 = I_1 + I_2 + I_3$$

$$\frac{V}{R} \text{ at } I_1 = \frac{V_A - 0}{2}$$


$$\frac{V}{R} \text{ at } I_2 = \frac{V_A - V_C}{2}$$
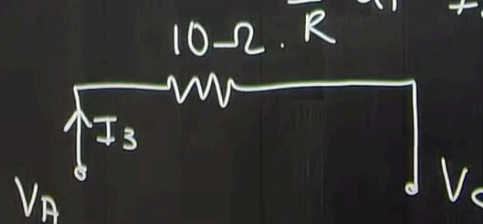
$$\frac{V}{R} \text{ at } I_3 = \frac{V_A - V_C}{10}$$





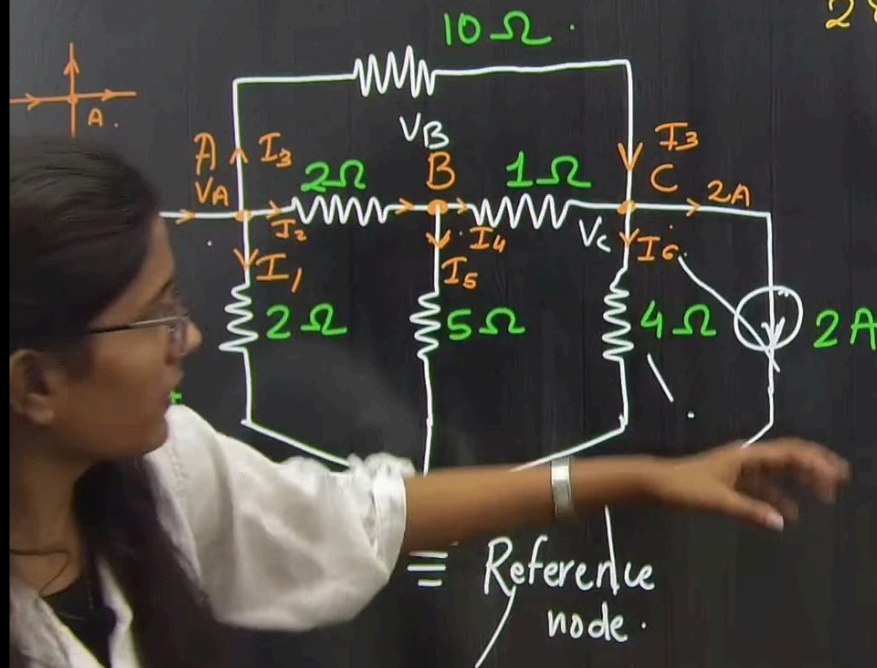find the current in various resistors of the circuit.



Apply KCL at node A.

$$28 = I_1 + I_2 + I_3$$

$$28 = \frac{V_A - 0}{2} + \frac{V_A - V_B}{2} + \frac{V_A - V_C}{10}$$


$$\frac{V}{R} \text{ at } I_1 = \frac{V_A - 0}{2}$$

$$\frac{V}{R} \text{ at } I_2 = \frac{V_A - V_B}{2}$$

$$\frac{V}{R} \text{ at } I_3 = \frac{V_A - V_C}{10}$$

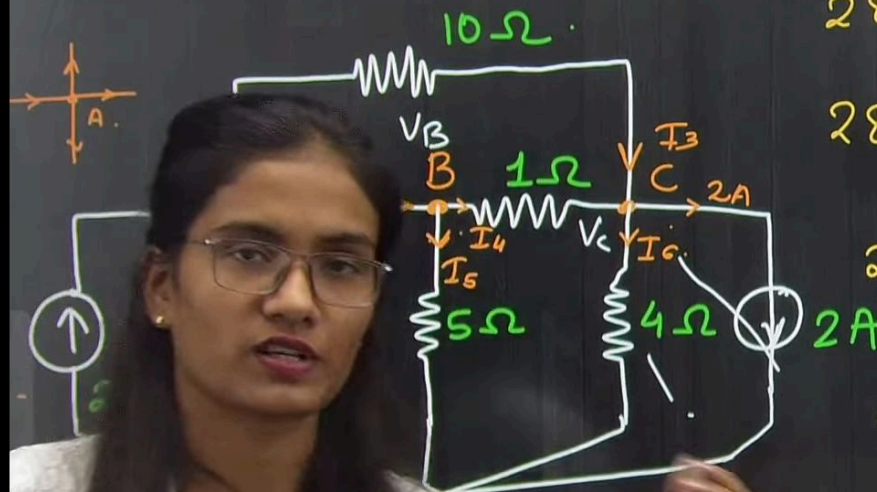08:08

find the current in various resistors of the circuit.



Reference node

Apply KCL at node A

08:10

$$28 = I_1 + I_2 + I_3$$


$$28 = \frac{V_A - 0}{2} + \frac{V_A - V_B}{2} + \frac{V_A - V_C}{10}$$

$$28 = \frac{(V_A) 5}{2 \times 5} + \frac{(V_A - V_B) \times 5}{2 \times 5} + \frac{V_A - V_C}{10}$$

$$28 = \frac{5V_A + 5V_A - 5V_B + V_A - V_C}{10}$$

$$28 \times 10 = 5V_A + 5V_A + V_A - 5V_B - V_C$$

$$11V_A - 5V_B - V_C = 280$$

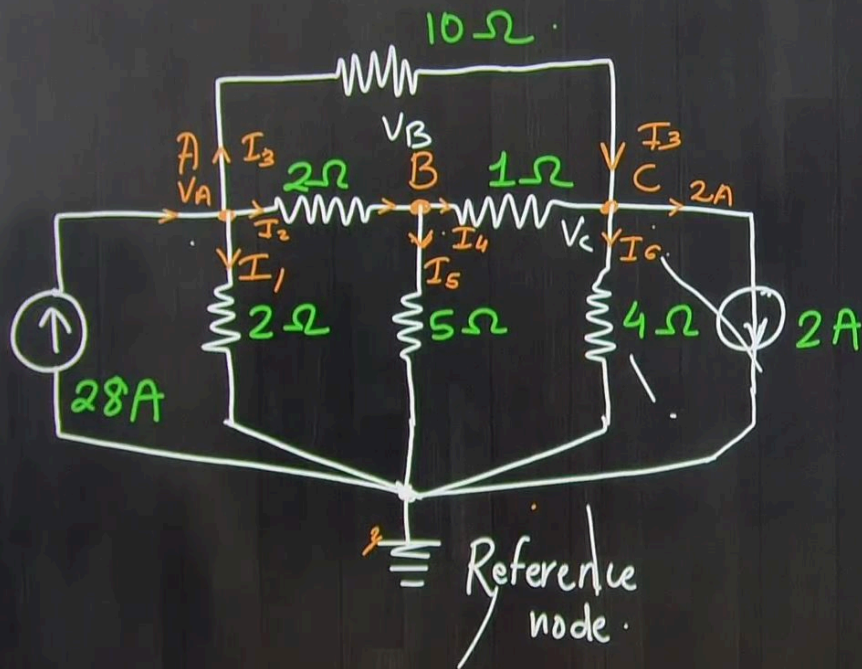

$$11V_A - 5V_B - V_C = 280 \quad \text{--- ①}$$

Apply KCL at node B.

$$I_2 = I_4 + I_5$$

$$\frac{V_A - V_B}{2} = \frac{V_B - V_C}{1} + \frac{V_B - 0}{5}$$


$$\frac{V_A - V_B}{2} = \frac{(V_B - V_C) \times 5 + \frac{V_B}{5}}{1 \times 5}$$

$$\frac{V_A - V_B}{2} = \frac{5V_B - 5V_C + V_B}{5}$$

$$\frac{V_A - V_B}{2} = \frac{6V_B - 5V_C}{5}$$

$$5(V_A - V_B) = 2(6V_B - 5V_C)$$



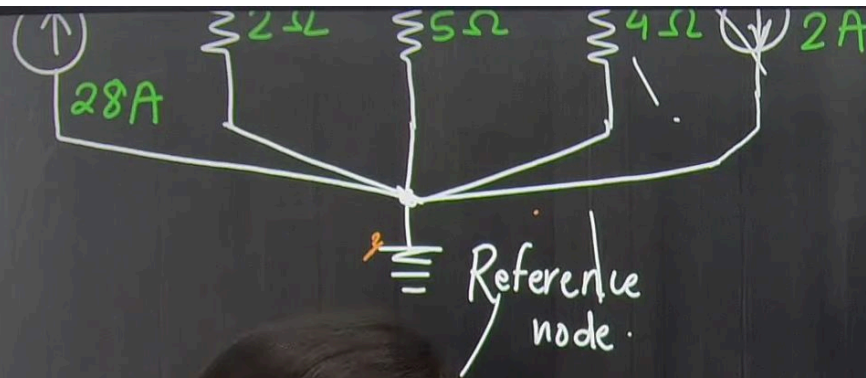

$$\frac{V_A - V_B}{2} = \frac{(V_B - V_C) \times 5}{1 \times 5} + \frac{V_B}{5}$$

$$\frac{V_A - V_B}{2} = \frac{5V_B - 5V_C + V_B}{5}$$

$$\frac{V_A - V_B}{2} = \frac{6V_B - 5V_C}{5}$$


$$5(V_A - V_B) = 2(6V_B - 5V_C)$$

$$5V_A - 5V_B = 12V_B - 10V_C$$

$$5V_A - 5V_B - 12V_B + 10V_C = 0$$
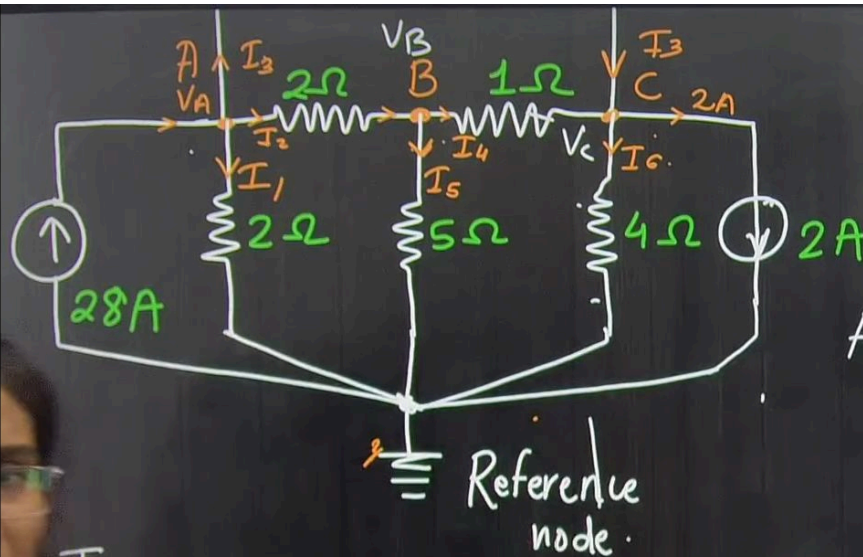
$$5V_A - 17V_B + 10V_C = 0 \quad \text{--- (2)}$$





$$I_1 =$$

$$5V_A - 5V_B = 12V_B - 10V_C$$

$$5V_A - 5V_B - 12V_B + 10V_C = 0$$

$$5V_A - 17V_B + 10V_C = 0 \quad (2)$$

Apply KCL at node  $V_C$ .

$$I_4 + I_3 = I_6 + 2$$

$$\frac{V_B - V_C}{1} + \frac{V_A - V_C}{10} = \frac{V_C - 0}{4} + 2$$


$$V_A + 10V_B - 13.5V_C = 20 \quad (3)$$

$$x = V_A = 36V$$

$$y = V_B = 20V$$

$$z = V_C = 16V$$

08:28

 Reference node.

$$I_1 = \frac{V_A}{2} = \frac{36}{2} = 18A //$$

$$I_2 = \frac{V_A - V_B}{2} = \frac{36 - 20}{2} = 8A.$$

$$I_3 = \frac{V_A - V_C}{10} = \frac{36 - 16}{10} = 2A.$$

$$I_4 = \frac{V_B - V_C}{1} = \frac{20 - 16}{1} = 4A$$

$$I_5 = \frac{V_B - 0}{5} = \frac{20 - 0}{5} = 4A.$$

$$I_6 = \frac{V_C - 0}{4} = \frac{16 - 0}{4} = 4A.$$

$$I_4 + I_3 = I_6 + 2.$$

$$\frac{V_B - V_C}{1} + \frac{V_A - V_C}{10} = \frac{V_C - 0}{4} + 2.$$

$$V_A + 10V_B - 13.5V_C = 20 \quad \text{--- (3)}$$

$$x = V_A = 36V$$

$$y = V_B = 20V$$

$$z = V_C = 16V$$

08:31

# Maximum Power Transfer Theorem

> Find the value of resistance  $R_L$  for maximum Power Transfer also calculate Maximum Power




Step 1: calculate  $V_{th}$   
by replacing  $R_L$  with  $V_{th}$   
and solve like nodal Analysis.

Step 2: Calculate  $R_{th}$   
By replacing  
Voltage source  $\rightarrow$  Short circuit  
Current source  $\rightarrow$  Open circuit  
Solve further till single resistance

Step 3:  $R_L = R_{th}$

Step 4: Calculate  $P_{max}$

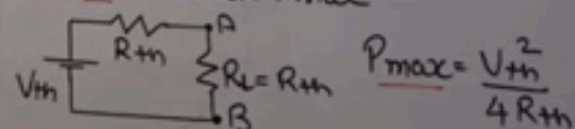

Nodal Analysis

Step 1: Identify Nodes

Step 2: Identify Equipotential nodes

Step 3: Identify the ground node

Step 4: Solve using formula

Formula:


Jahase Nikal raha hai  
- Jahape Joota hai  
+/- V

Resistance




> Find the value of resistance  $R_L$  for maximum Power Transfer also calculate Maximum Power

Applying KCL to VA

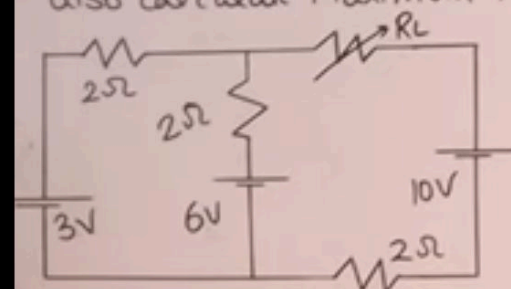

Step 1: calculating  $V_{th}$

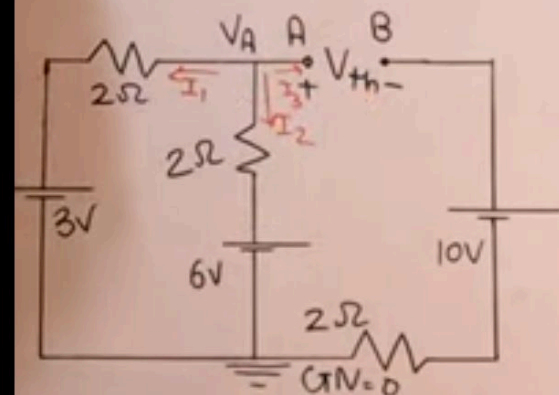


Step 1: calculate  $V_{th}$  by replacing  $R_L$  with  $V_{th}$  and solve like nodal analysis.

Step 2: Calculate  $R_{th}$  By replacing Voltage source  $\rightarrow$  Short circuit Current source  $\rightarrow$  Open circuit Solve further till single resistance

Step 3:  $R_L = R_{th}$

Step 4: Calculate  $P_{max}$

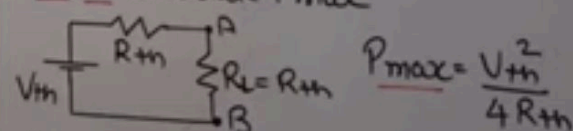

Nodal Analysis

Step 1: Identify Nodes

Step 2: Identify Equipotential nodes

Step 3: Identify the ground node


Step 4: Solve using formula

Formula:


Jahase Nikal raha hai  
- Jahape Jaoraha hai  
+/- V

Resistance

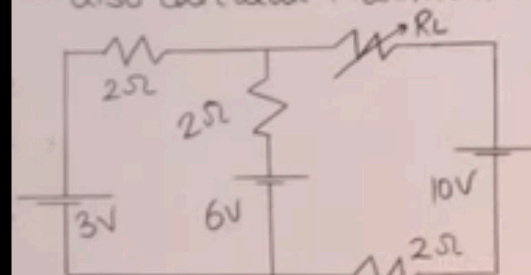⇒ Find the value of resistance  $R_L$  for maximum Power Transfer also calculate Maximum Power



Step 1: calculating  $V_{th}$

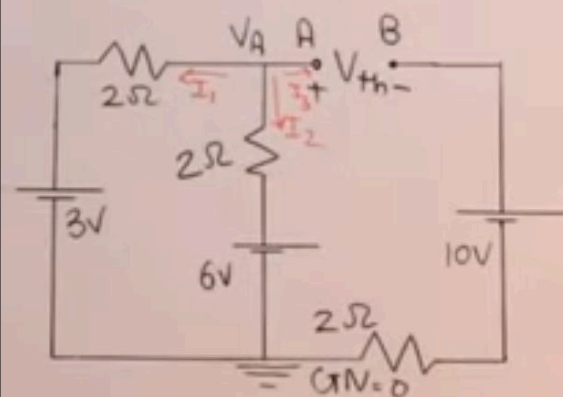

Applying KCL to  $V_A$

$$\frac{V_A - 3}{2} + \frac{V_A - 6}{2} = 0$$

$$\frac{V_A - 3 + V_A - 6}{2} = 0$$

$$2V_A - 9 = 0$$

$$V_A = \frac{9}{2} = 4.5V$$

Writing eq<sup>n</sup> for  $V_{th}$

$$V_A - V_{th} - 10 = 0$$


$$V_{th} = V_A - 10$$

$$= 4.5 - 10$$


$$= -5.5$$

$$= 5.5 \text{ (terminal B is + w.r.t A)}$$

Step 2: calculate  $R_{th}$

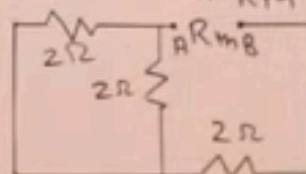

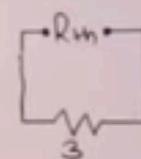
$$2 \parallel 2 = 2 \times 2 / 2 + 2 = 1$$



$$R_{th} = 1 + 2 = 3\Omega$$

Step 3:  $R_L = R_{th} = 3\Omega$

Step 4: calculate  $P_{max}$

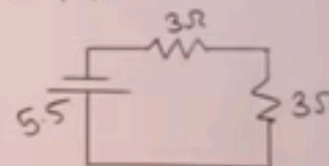

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{(5.5)^2}{4(3)}$$

$$= 2.52W$$