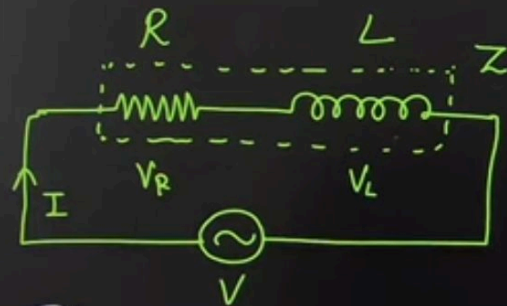



AC Circuits

- Resistance^R, Inductance and Capacitance
- Addition of current and voltage requires phase difference
- Phase angle (ϕ)
 - nature of circuit [Resistive, inductive, capacitive]
 - circuit impedance
 - power consumed.


RL Series Circuit



Phasor diagram.

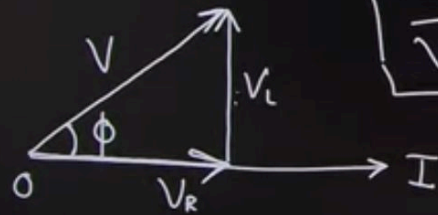

$$\vec{V} = \vec{V}_R + \vec{V}_L$$

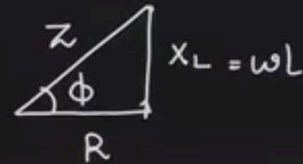

$$Z = \sqrt{R^2 + X_L^2}$$

$$\phi = \tan^{-1}\left(\frac{V_L}{V_R}\right) \quad \phi = \tan^{-1}\left(\frac{X_L}{R}\right)$$

$$\bar{Z} = (R + jX_L)$$

$$\bar{Z} = (Z \angle \phi)$$

Ohms law

$$V = IZ$$


$$V_R = IR$$

$$V_L = IX_L$$

Inductance $\begin{cases} V_L \text{ leads } I \text{ by } \pi/2 \\ I \text{ lags } V_L \text{ by } \pi/2 \end{cases}$

$$\frac{P_{rms}}{V_{rms}}$$

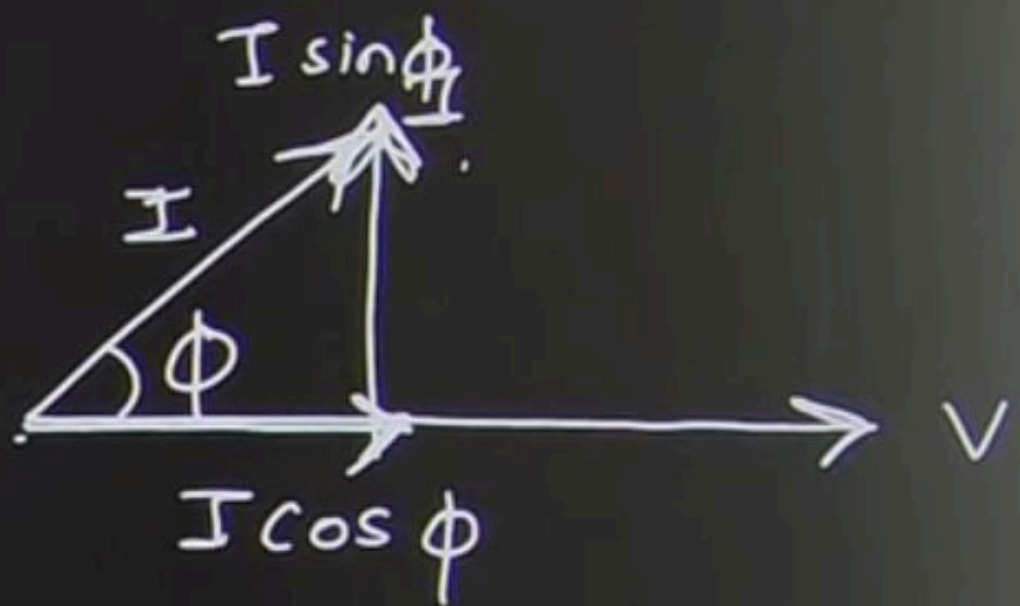power factor $\cos \phi = \frac{R}{Z}$ [lagging]



Active power

$$(\text{consumable}) = V \times I \cos \phi$$



wl

$$\text{Reactive power} = V \times I \sin \phi$$

✓

$$\text{Apparent power} = V \times I$$

R-C Series Circuit

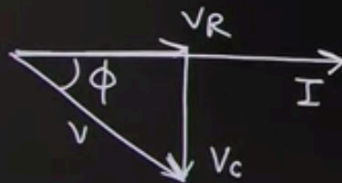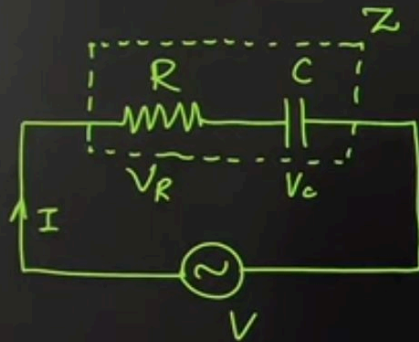

$$\bar{V} = \bar{V}_R + \bar{V}_C$$

$$\phi = \tan^{-1} \left(\frac{V_C}{V_R} \right)$$

By ohm's law.


$$V = IZ$$

$$V_R = IR \quad X_C = \frac{1}{\omega C}$$


$$V_C = IX_C$$

I leads voltage.

Voltage Δ

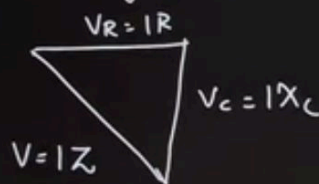

Impedance Δ

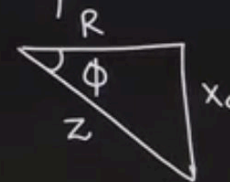

$$Z = \sqrt{R^2 + X_C^2}$$

$$\phi = \tan^{-1} \left(\frac{X_C}{R} \right)$$


$$\bar{Z} = (R - jX_C) \Omega$$

$$\bar{Z} = (Z \angle -\phi)$$

Power factor

$$\cos \phi = \frac{R}{Z} \text{ (leading)}$$

Power Δ

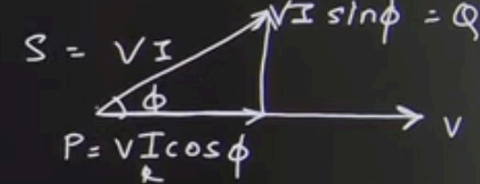


Active power $P = VI \cos \phi$ (KW)

Reactive power $Q = VI \sin \phi$ (KVAR)

Apparent power $S = VI$ KVA

R-L-C Series Circuit

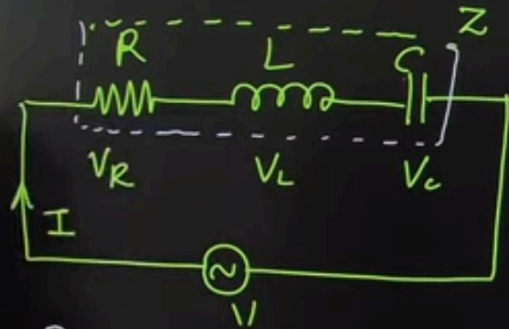

By Ohm's law

$$V = IZ$$

$$V_R = IR$$


$$V_L = IX_L$$

$$V_C = IX_C$$

R-L-C Series Circuit

Case 1. $X_L > X_C$
 $V_L > V_C$

Phasor diagram.

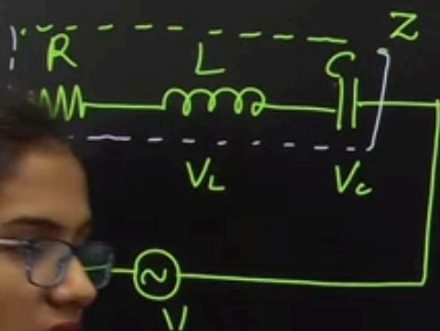


Ohm's law

$$V = IZ$$


$$V_R = IR$$

$$V_L = IX_L$$

$$V_C = IX_C$$

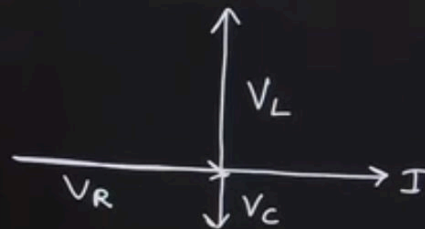

R-L-C Series Circuit

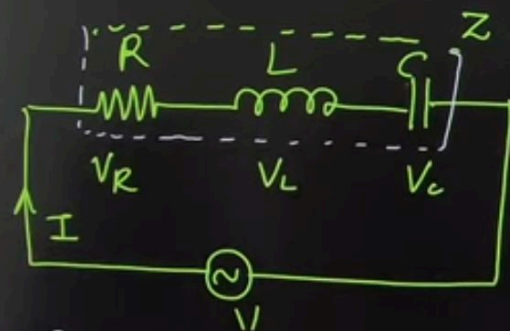

By Ohm's law

$$V = IZ$$


$$V_R = IR$$

$$V_L = IX_L$$


$$V_C = IX_C$$

Case 1. $X_L > X_C$
 $V_L > V_C$

Phasor diagram.

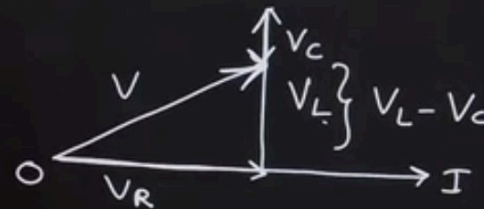

R-L-C Series Circuit

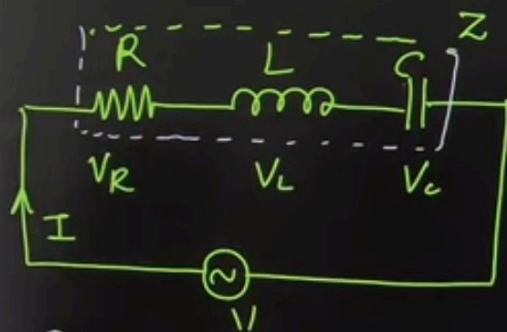

By Ohm's law

$$V = IZ$$

$$V_R = IR$$




$$V_L = IX_L$$

$$V_C = IX_C$$

Case 1. Inductive > Capacitive
 $X_L > X_C$
 $V_L > V_C$

lagging \rightarrow Power factor $\cos \phi = \frac{R}{Z}$

Phasor diagram.

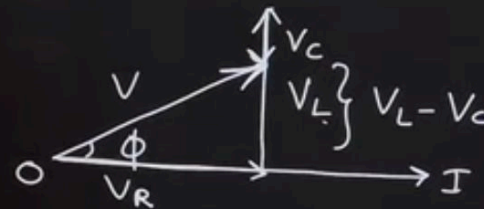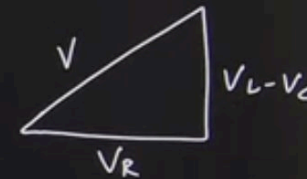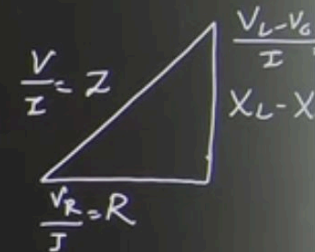Voltage Δ Impedance Δ 

$$\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C$$

$$\phi = \tan^{-1} \left(\frac{V_L - V_C}{V_R} \right)$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$


$$\bar{Z} = R + j(X_L - X_C) \Omega$$

$$\bar{Z} = (Z \angle \phi)$$

$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

R-L-C - Series Circuit

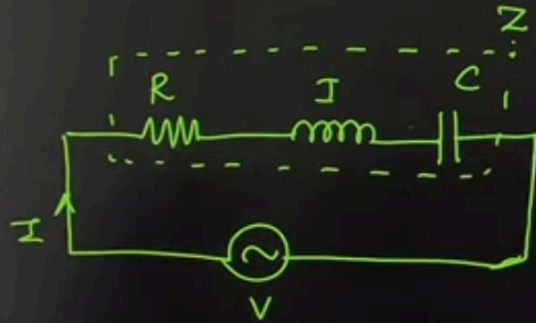

By ohm's law.

$$V_R = IR$$


$$V_L = I X_L$$

$$V_C = I X_C$$

$$V = IZ$$

Case 2: $X_C > X_L$
 $V_C > V_L$

Phasor diagram.

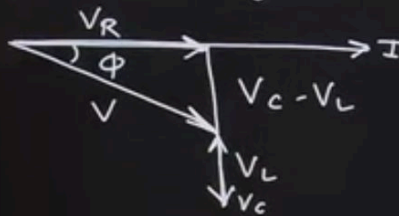


$$\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C$$

$$\phi = \tan^{-1} \left(\frac{V_C - V_L}{V_R} \right)$$


$$\phi = \tan^{-1} \left(\frac{X_C - X_L}{R} \right)$$

Power factor $\cos \phi = \frac{R}{Z}$ leading

Voltage Δ

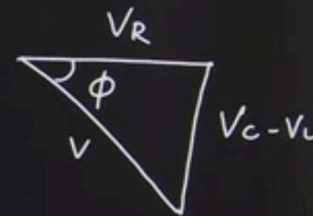

Impedance Δ

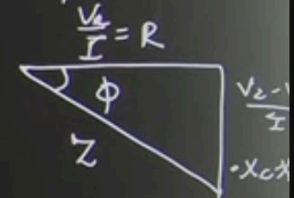

$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$\bar{Z} = R - j(X_C - X_L) \Omega$$

$$\bar{Z} = (Z \angle \phi)$$

$$X_C = \frac{1}{\omega C}$$

$$X_L = \omega L$$