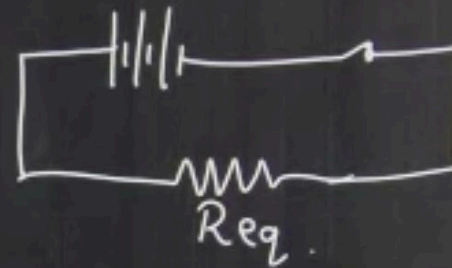


What is equivalent circuit?

If more than two passive elements are connected in any combination then the combined effect of the connection can be represented by single equivalent passive element in the same circuit.




Hence the circuit is known as equivalent circuit.



Series equivalent

Parallel equivalent


Series + Parallel

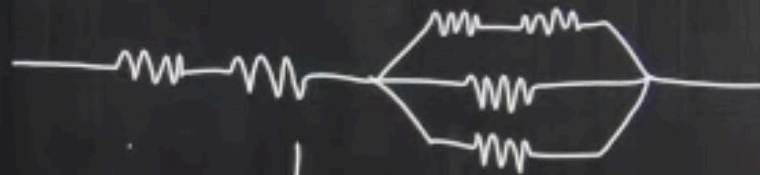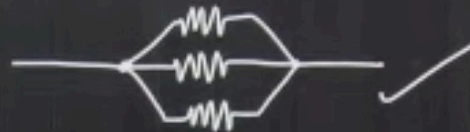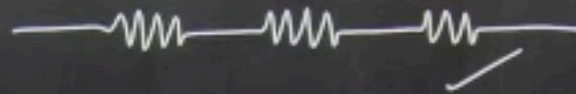

↓  
Star delta transformation,


Series Equivalent circuit (R/L/C).

09:50

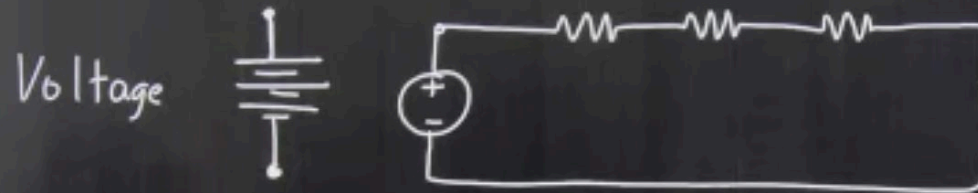

Series Equivalent circuit (R/L/C).

09:54

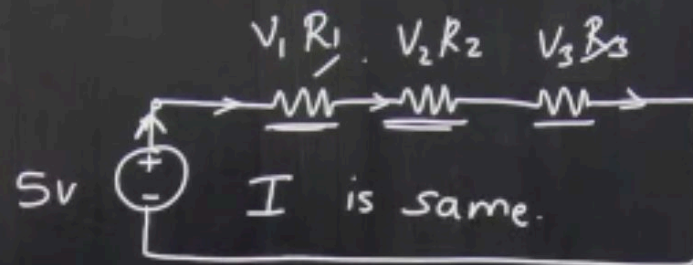


Voltage is different  
for each passive  
element (Resistor).  
∴

KVL.

$$S_v = V_1 + V_2 + V_3.$$

Series Equivalent circuit (R/L/C).

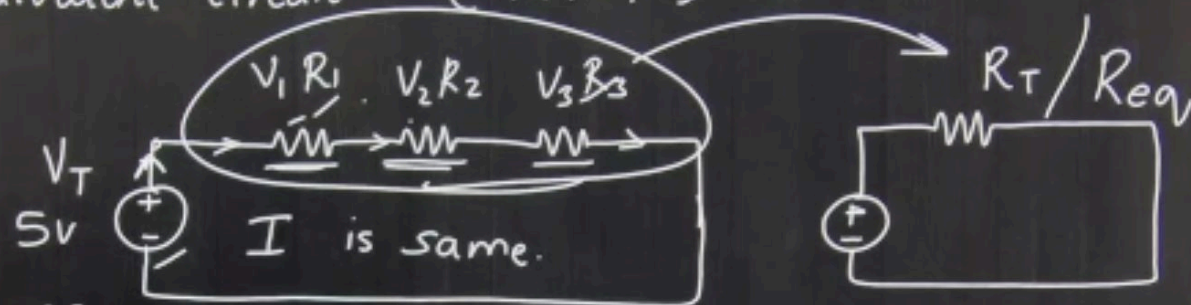

voltage is different  
for each passive  
element (Resistors).

KVL.

$$SV = V_1 + V_2 + V_3.$$

$$V_T = V_1 + V_2 + V_3 \quad \text{[by KVL]}$$

$$IR_T = IR_1 + IR_2 + IR_3$$

$$IR_T = I(R_1 + R_2 + R_3) \quad \begin{matrix} V \propto I \\ V = IR \text{ — by ohm's law} \end{matrix}$$

$$R_T = R_1 + R_2 + R_3$$




$$SV = V_1 + V_2 + V_3$$

$$R_T = R_1 + R_2 + R_3 \dots R_n$$

10:01

When Inductors are connected in series

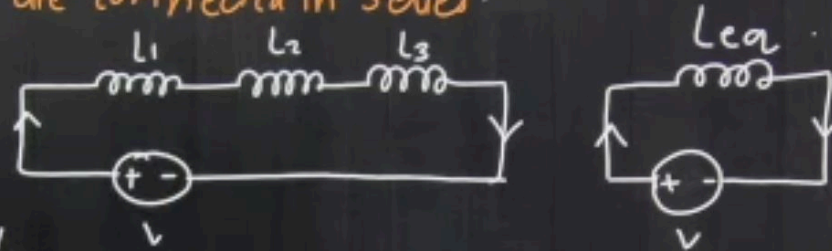


$$L_{eq} / L_T = L_1 + L_2 + L_3 \dots L_n$$

When Capacitor is connected in series

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_n}$$

# Parallel Equivalent Circuit

When resistor is connected in parallel

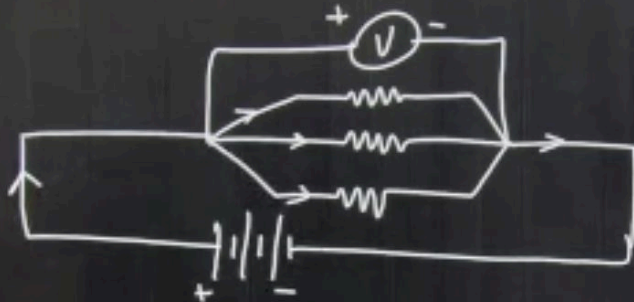


Voltage remains same  $\rightarrow$  Current is divided.

$$I_s = I_1 + I_2 + I_3$$


$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$
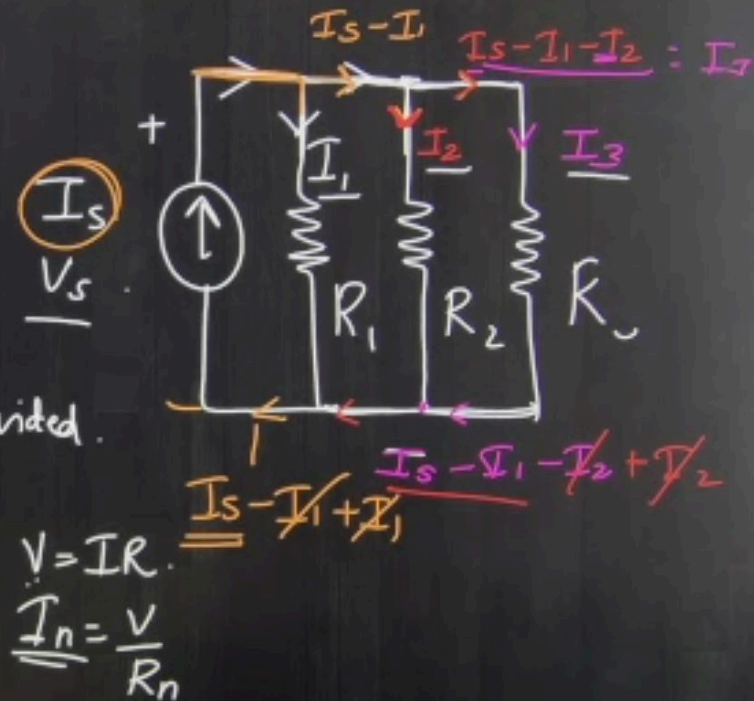
$$\frac{V}{R_{eq}} = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$




$$V = IR$$

$$I_n = \frac{V}{R_n}$$

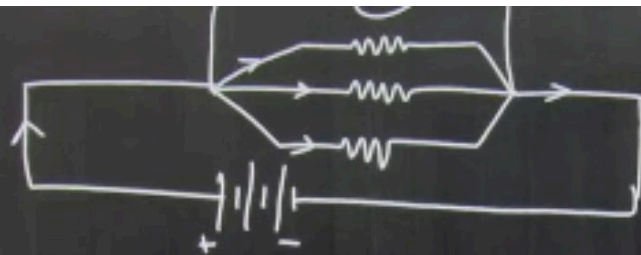
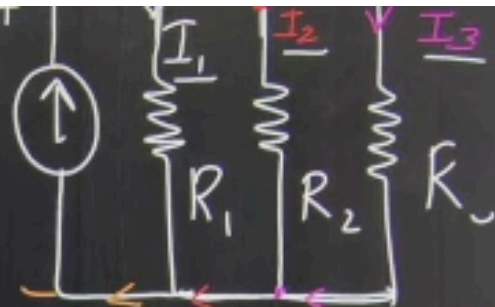
$$\begin{matrix} I_s \\ V_s \end{matrix}$$



10:12

Voltage remains same  $\rightarrow$  Current is divided.

$$I_s = I_1 + I_2 + I_3$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$


$$\frac{V}{R_{eq}} = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$V = IR$$

$$I_n = \frac{V}{R_n}$$

$$I_s - I_1 - I_2 + I_2$$

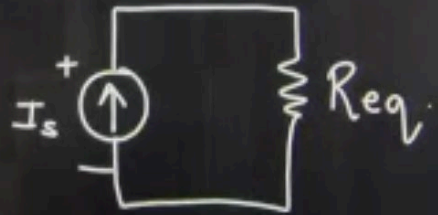




$$\frac{V}{R_{eq}} = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$R_n$

$$\mathcal{E}I = 0$$

10:15

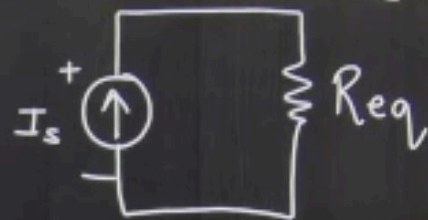


When inductor is connected (Magnetic flux).

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \dots$$

When capacitor is connected (Stores electric).


$$C_{eq} = C_1 + C_2 + C_3 \dots$$

Q. find  $R_{eq}$  of circuit.

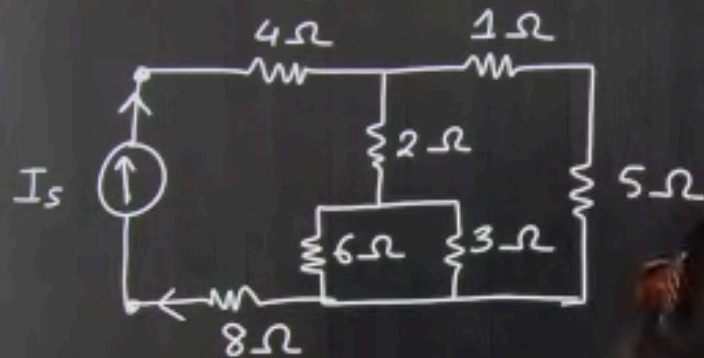


① Extreme point

② Series continuous

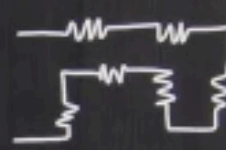

or parallel


Joining

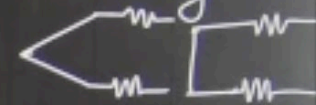

③  $R_{eq}$

Series  $\rightarrow R_1 + R_2 + R_3 \dots$

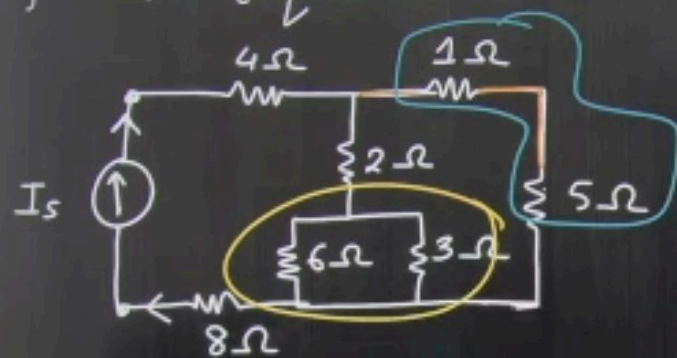Parallel  $\rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$




$$1\Omega + 5\Omega = 6\Omega \text{ [Series]}$$

$$6\Omega \parallel 3\Omega$$


$$\frac{1}{R_{eq}} = \frac{1}{6} + \frac{1}{3}$$

$$\frac{1}{R_{eq}} = \frac{1}{2}$$

$$R_{eq} = 2 \quad \text{reciprocal.}$$

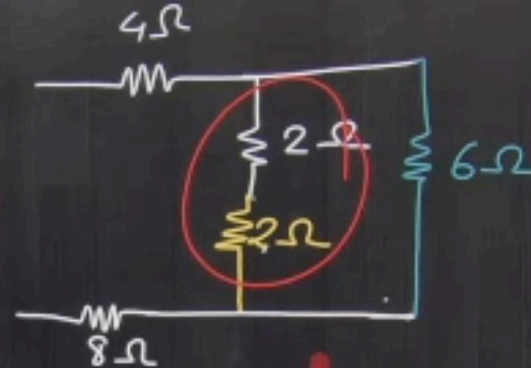

$$2 + 2 = 4\Omega$$

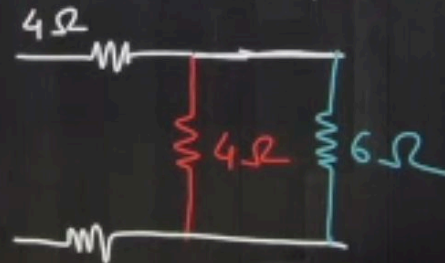

① 100%

② Se


contin

③ Req

Series

Parallel

$\Omega$  [Series]  $2+2=4\Omega$

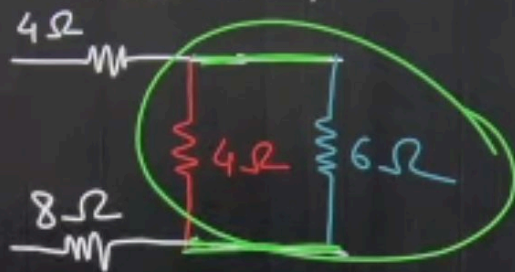

uprod.


$6\Omega || 4\Omega$

$$\frac{1}{R_{eq}} = \frac{1}{6} + \frac{1}{4}$$

$$\frac{1}{R_{eq}} = \frac{5}{12}$$

$$R_{eq} = \frac{12}{5}$$

reciprocal

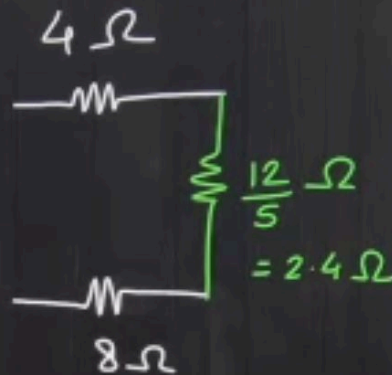

$$R_{eq} = 4 + 2.4 + 8$$
$$= 14.4\Omega$$

Series  $\rightarrow R_1 + R_2 + R_3 \dots$

Parallel  $\rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

10:32